

Table of Contents

AND GATE (Dataflow & Behavioral Model)	2
OR GATE (Dataflow & Behavioral Model)	8
NOT GATE (Dataflow & Behavioral Model)	14
NAND GATE (Dataflow & Behavioral Model)	19
NOR GATE (Dataflow & Behavioral Model)	25
XOR GATE (Dataflow & Behavioral Model)	31
XNOR GATE (Dataflow & Behavioral Model)	37
AND GATE using NAND GATE	43
OR GATE using NAND GATE	46
NOT GATE using NAND GATE	49
XOR GATE using NAND GATE	51
XNOR GATE using NAND GATE	54
AND GATE using NOR GATE	57
OR GATE using NOR GATE	60
NOT GATE using NOR GATE	63
XOR GATE using NOR GATE	65
XNOR GATE using NOR GATE	68
HALF ADDER (Dataflow, Behavioral & Structural Model)	71
FULL ADDER (Dataflow, Behavioral & Structural Model)	80
2:1 MUX (Dataflow & Behavioral Model)	91
4:1 MUX (Dataflow & Behavioral Model)	97
3:8 DECODER (Dataflow & Behavioral Model)	103

AND Gate Dataflow Model


VHD Code:

```
entity AND_DF is
    Port ( A : in STD_LOGIC;
           B : in STD_LOGIC;
           C : out STD_LOGIC);
end AND_DF;
architecture Dataflow of AND_DF is
begin

    C <= A AND B;

end Dataflow;
```

RTL Diagram

 

TBW Code:

```
entity AND_DF_TBW is
```

```
-- Port ( );
```

```
end AND_DF_TBW;
```

```
architecture Dataflow of AND_DF_TBW is
```

```
component AND_DF is
```

```
    Port ( A : in STD_LOGIC;
```

```
           B : in STD_LOGIC;
```

```
           C : out STD_LOGIC);
```

```
end component;
```

```
Signal a1:STD_LOGIC:='0';
```

```
Signal b1:STD_LOGIC:='0';
```

```
Signal c1:STD_LOGIC;
```

```
begin
```

```
UUT: AND_DF Port map(A=>a1, B=>b1, c=>c1);
```

```
stim_proc: process
```

```
begin
```

```
wait for 100ns;
```

```
a1<='0';
```

```
b1<='0';
```

```
wait for 100ns;
```

```
a1<='0';
```

```
b1<='1';
```

```
wait for 100ns;
```

```
a1<='1';
```

```
b1<='0';
```

```
wait for 100ns;
```

```
a1<='1';
```


```
b1<='1';
```

```
wait;
```

```
end process;
```

```
end Dataflow;
```

TBW Waveform

 

AND Gate Behavioral Model

VHD Code:

entity AND_GATE_BV is

Port (A : in STD_LOGIC;

B : in STD_LOGIC;

C : out STD_LOGIC);

end AND_GATE_BV;

architecture Behavioral of AND_GATE_BV is

begin

process(A,B)

begin

if(A='1' and B='1') then

c<='1';

else


c<='0';

end if;

end process;

end Behavioral;

RTL Diagram

 

TBW Code:

entity AND_GATE_TBW is

-- Port ();

end AND_GATE_TBW;

architecture Behavioral of AND_GATE_TBW is

component AND_GATE_BV is

Port (A : in STD_LOGIC;

B : in STD_LOGIC;

C : out STD_LOGIC);

end component;

Signal a1:STD_LOGIC:='0';

Signal b1:STD_LOGIC:='0';

Signal c1:STD_LOGIC;

begin

```
UUT: AND_GATE_BV Port map(A=>a1, B=>b1, C=>c1);
```

```
stim_proc: process
```

```
begin
```

```
wait for 100ns;
```

```
a1<='0';
```

```
b1<='0';
```

```
wait for 100ns;
```

```
a1<='0';
```

```
b1<='1';
```

```
wait for 100ns;
```

```
a1<='1';
```

```
b1<='0';
```

```
wait for 100ns;
```

```
a1<='1';
```


```
b1<='1';
```

```
wait;
```

```
end process;
```

```
end Behavioral;
```

TBW Waveform

 


OR Gate Dataflow Model

VHD Code:

```
entity OR_DF is
  Port ( a : in STD_LOGIC;
         b : in STD_LOGIC;
         c : out STD_LOGIC);
end OR_DF;

architecture Dataflow of OR_DF is
begin
  c <= a OR b;
end Dataflow;
```

RTL Diagram

 

TBW Code:

entity OR_DF_TBW is

-- Port ();

end OR_DF_TBW;

architecture Dataflow of OR_DF_TBW is

component OR_DF is

Port (a : in STD_LOGIC;

b : in STD_LOGIC;

c : out STD_LOGIC);

end component;

Signal a1:STD_LOGIC:='0';

Signal b1:STD_LOGIC:='0';

Signal c1:STD_LOGIC;

begin

UUT: OR_DF Port map(a=>a1, b=>b1, c=>c1);

stim_proc: process

begin

wait for 100ns;

a1<='0';

b1<='0';

wait for 100ns;

```

a1<='0';
b1<='1';

wait for 100ns;

a1<='1';
b1<='0';


wait for 100ns;

a1<='1';
b1<='1';

wait;
end process;
end Dataflow;

```

TBW Waveform

 


OR Gate Behavioral Model

VHD Code:

```
entity OR_GATE_BV is
    Port ( A : in STD_LOGIC;
           B : in STD_LOGIC;
           C : out STD_LOGIC);
end OR_GATE_BV;

architecture Behavioral of OR_GATE_BV is
begin
    process(A,B)
    begin
        if(A='0' and B='0') then
            c<='0';
        else
            c<='1';
        end if;
    end process;
end Behavioral;
```

RTL Diagram

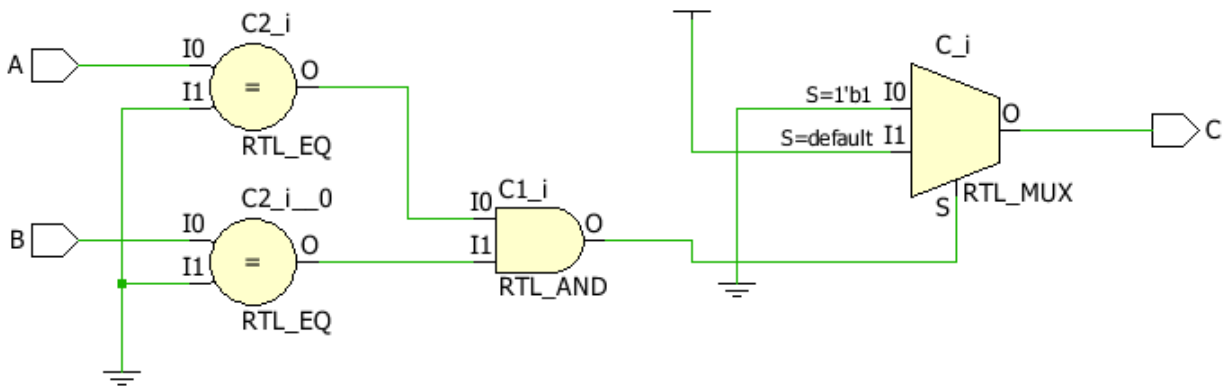

TBW Code:

entity OR_GATE_TBW is

-- Port ();

end OR_GATE_TBW;

architecture Behavioral of OR_GATE_TBW is

component OR_GATE_BV is

Port (a : in STD_LOGIC;

b : in STD_LOGIC;

c : out STD_LOGIC);

end component;

Signal a1:STD_LOGIC:='0';

Signal b1:STD_LOGIC:='0';

Signal c1:STD_LOGIC;

begin

```
UUT: OR_GATE_BV Port map(a=>a1, b=>b1, c=>c1);
```

```
stim_proc: process
```

```
begin
```

```
wait for 100ns;
```

```
a1<='0';
```

```
b1<='0';
```

```
wait for 100ns;
```

```
a1<='0';
```

```
b1<='1';
```

```
wait for 100ns;
```

```
a1<='1';
```

```
b1<='0';
```

```
wait for 100ns;
```

```
a1<='1';
```


```
b1<='1';
```

```
wait;
```

```
end process;
```

```
end Behavioral;
```

TBW Waveform

 


NOT Gate Dataflow Model

VHD Code:

```
entity NOT_DF is
    Port ( a : in STD_LOGIC;
           b : out STD_LOGIC);
end NOT_DF;
architecture Dataflow of NOT_DF is
begin
    b <= NOT a;
end Dataflow;
```

RTL Diagram

 

TBW Code:

```
entity NOT_DF_TBW is
-- Port ( );
```

```

end NOT_DF_TBW;

architecture Dataflow of NOT_DF_TBW is
component NOT_DF is
    Port ( a : in STD_LOGIC;
           b : out STD_LOGIC);
end component;

Signal a1:STD_LOGIC:='0';
Signal b1:STD_LOGIC;


begin

UUT: NOT_DF Port map(a=>a1, b=>b1);

stim_proc: process
begin
wait for 100ns;
a1<='0';
wait for 100ns;
a1<='1';
wait;
end process;
end Dataflow;

```

TBW Waveform

 


NOT Gate Behavioral Model

VHD Code:

```
entity NOT_GATE_BV is
    Port ( A : in STD_LOGIC;
           B : out STD_LOGIC);
end NOT_GATE_BV;

architecture Behavioral of NOT_GATE_BV is
begin
    process(A)
    begin
        if(A='0') then
            B<='1';
        else
            B<='0';
        end if;
    end process;
end Behavioral;
```


RTL Diagram

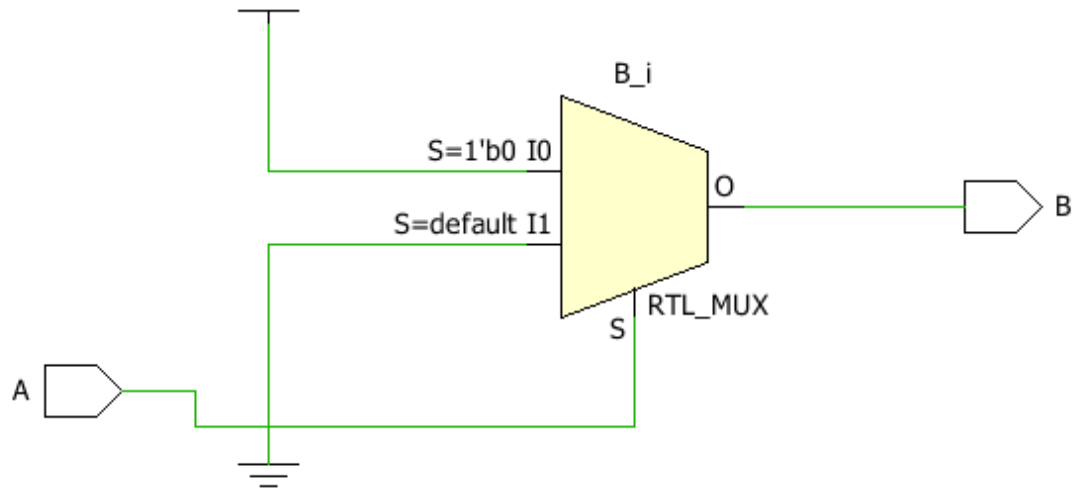

TBW Code:

```
entity NOT_GATE_TBW is
-- Port ( );
end NOT_GATE_TBW;

architecture Behavioral of NOT_GATE_TBW is
component NOT_GATE_BV is
    Port ( a : in STD_LOGIC;
          b : out STD_LOGIC);
end component;


Signal a1:STD_LOGIC:='0';
Signal b1:STD_LOGIC;
```

```

begin
UUT: NOT_GATE_BV Port map(a=>a1, b=>b1);
stim_proc: process
begin
wait for 100ns;
a1<='0';
wait for 100ns;
a1<='1';
wait;
end process;
end Behavioral;

```

TBW Waveform

 

NAND Gate Dataflow Model

VHD Code:

```
entity NAND_DF is
    Port ( a : in STD_LOGIC;
           b : in STD_LOGIC;
           c : out STD_LOGIC);
end NAND_DF;

architecture Dataflow of NAND_DF is
begin
    c<=a NAND b;
end Dataflow;
```

RTL Diagram



TBW Code:

```
entity NAND_DF_TBW is
-- Port ( );
end NAND_DF_TBW;
```

architecture Dataflow of NAND_DF_TBW is

component NAND_DF is

```
Port ( a : in STD_LOGIC;  
       b : in STD_LOGIC;  
       c : out STD_LOGIC);
```

end component;

Signal a1:STD_LOGIC:='0';

Signal b1:STD_LOGIC:='0';

Signal c1:STD_LOGIC;

begin

UUT: NAND_DF Port map(a=>a1, b=>b1, c=>c1);

stim_proc: process

begin

wait for 100ns;

a1<='0';

b1<='0';

wait for 100ns;

a1<='0';

b1<='1';

wait for 100ns;

a1<='1';

b1<='0';

wait for 100ns;


a1<='1';

b1<='1';

wait;

```
end process;  
end Dataflow;
```

TBW Waveform

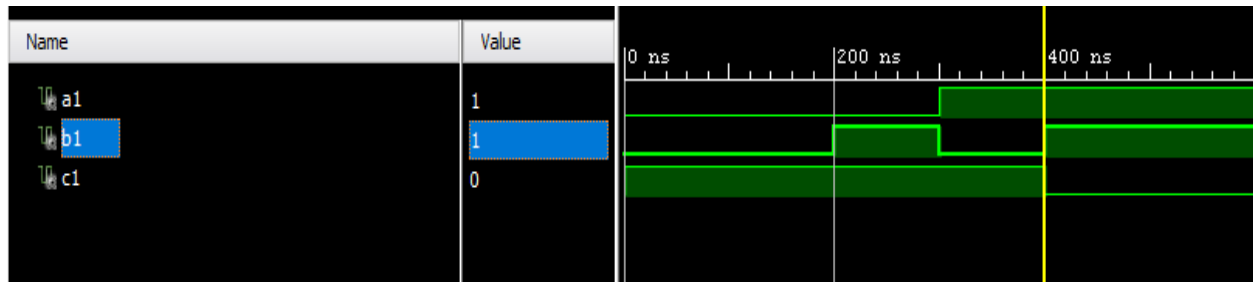


NAND Gate Behavioral Model

VHD Code:

```
entity NAND_GATE_BV is
    Port ( A : in STD_LOGIC;
           B : in STD_LOGIC;
           C : out STD_LOGIC);
end NAND_GATE_BV;

architecture Behavioral of NAND_GATE_BV is
begin
    process(A,B)
    begin
        if(A='1' and B='1') then
            c<='0';
        else
            c<='1';
        end if;
    end process;
end Behavioral;
```

RTL Diagram

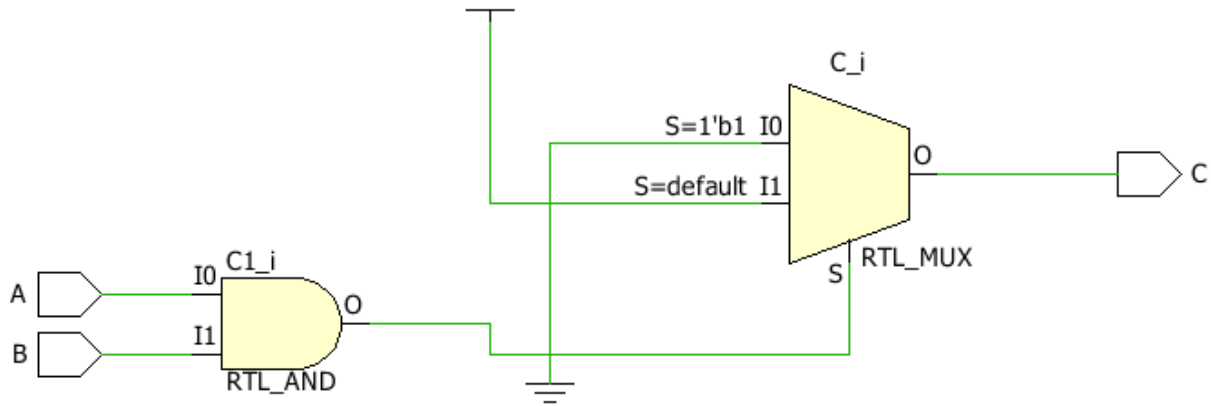

TBW Code:

entity NAND_GATE_TBW is

-- Port ();

end NAND_GATE_TBW;

architecture Dataflow of NAND_GATE_TBW is

component NAND_GATE_BV is

Port (a : in STD_LOGIC;

b : in STD_LOGIC;

c : out STD_LOGIC);

end component;

Signal a1:STD_LOGIC:='0';

Signal b1:STD_LOGIC:='0';

Signal c1:STD_LOGIC;

begin

UUT: NAND_GATE_BV Port map(a=>a1, b=>b1, c=>c1);

stim_proc: process


begin

```

wait for 100ns;
a1<='0';
b1<='0';
wait for 100ns;
a1<='0';
b1<='1';
wait for 100ns;
a1<='1';
b1<='0';
wait for 100ns;
a1<='1';
b1<='1';
wait;
end process;
end Dataflow;

```

TBW Waveform

 

NOR Gate Dataflow Model

VHD Code:

entity NOR_DF is

Port (a : in STD_LOGIC;

b : in STD_LOGIC;

c : out STD_LOGIC);

end NOR_DF;

architecture Dataflow of NOR_DF is

begin

c<=a NOR b;

end Dataflow;

RTL Diagram



TBW Code:

entity NOR_DF_TBW is

-- Port ();

end NOR_DF_TBW;

architecture Dataflow of NOR_DF_TBW is

component NOR_DF is

Port (a : in STD_LOGIC;

b : in STD_LOGIC;

c : out STD_LOGIC);

end component;

Signal a1:STD_LOGIC:='0';

Signal b1:STD_LOGIC:='0';

Signal c1:STD_LOGIC;

begin

UUT: NOR_DF Port map(a=>a1, b=>b1, c=>c1);

stim_proc: process

begin

wait for 100ns;

a1<='0';

b1<='0';

wait for 100ns;

a1<='0';

b1<='1';

wait for 100ns;

a1<='1';

b1<='0';

```
wait for 100ns;
```

```
a1<='1';
```


```
b1<='1';
```

```
wait;
```

```
end process;
```

```
end Dataflow;
```

TBW Waveform

 

NOR Gate Behavioral Model


VHD Code:

```
entity NOR_GATE_BV is
```

```
    Port ( A : in STD_LOGIC;
```

```
B : in STD_LOGIC;  
C : out STD_LOGIC);  
end NOR_GATE_BV;  
architecture Behavioral of NOR_GATE_BV is  
begin  
process(A,B)  
begin  
    if(A='0' and B='0') then  
        C<='1';  
    else  
        C<='0';  
    end if;  
end process;  
end Behavioral;
```

RTL Diagram

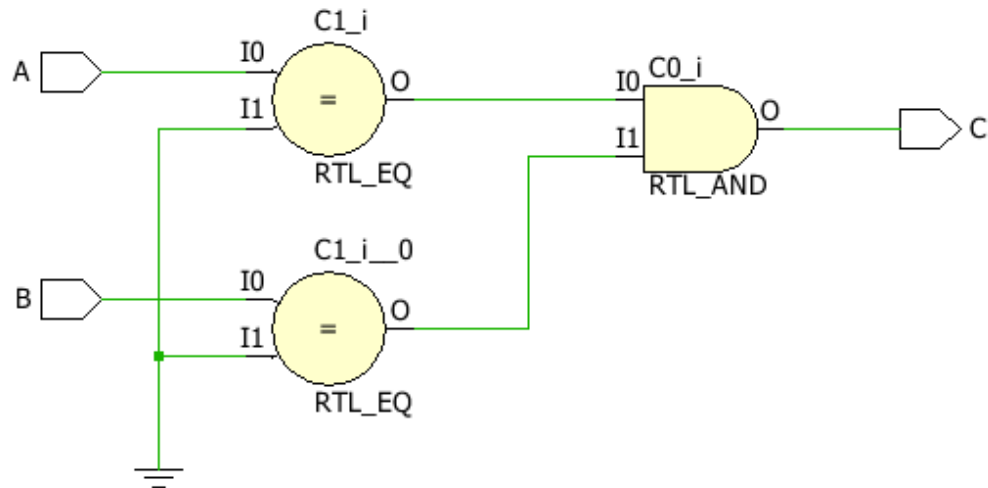

TBW Code:

entity NOR_GATE_TBW is

-- Port ();

end NOR_GATE_TBW;

architecture Behavioral of NOR_GATE_TBW is

component NOR_GATE_BV is

Port (A : in STD_LOGIC;

B : in STD_LOGIC;

C : out STD_LOGIC);

end component;

Signal a1:STD_LOGIC:= '0';

Signal b1:STD_LOGIC:= '0';

Signal c1:STD_LOGIC;

begin

UUT: NOR_GATE_BV Port map(A=>a1, B=>b1, C=>c1);


stim_proc: process

```

begin
wait for 100ns;
a1<='0';
b1<='0';
wait for 100ns;
a1<='0';
b1<='1';
wait for 100ns;
a1<='1';
b1<='0';
wait for 100ns;
a1<='1';
b1<='1';
wait;
end process;
end Behavioral;

```

TBW Waveform

 

XOR Gate Dataflow Model

VHD Code:

entity XOR_DF is

```
    Port ( a : in STD_LOGIC;  
          b : in STD_LOGIC;  
          c : out STD_LOGIC);
```

end XOR_DF;


architecture Dataflow of XOR_DF is

begin

```
c<=a XOR b;
```

end Dataflow;

RTL Diagram

 

TBW Code:

```
entity XOR_DF_TBW is
```

```
-- Port ( );
```

```
end XOR_DF_TBW;
```

```
architecture Dataflow of XOR_DF_TBW is
```

```
component XOR_DF is
```

```
    Port ( a : in STD_LOGIC;
```

```
          b : in STD_LOGIC;
```

```
          c : out STD_LOGIC);
```

```
end component;
```

```
Signal a1:STD_LOGIC:='0';
```

```
Signal b1:STD_LOGIC:='0';
```

```
Signal c1:STD_LOGIC;
```

```
begin
```

```
UUT: XOR_DF Port map(a=>a1, b=>b1, c=>c1);
```

```
stim_proc: process
```

```
begin
```

```
wait for 100ns;
```

```
a1<='0';
```

```
b1<='0';
```

```
wait for 100ns;
```

```
a1<='0';
```

```
b1<='1';
```



```
wait for 100ns;
```

```
a1<='1';
```

```
b1<='0';
```

```
wait for 100ns;
```

```
a1<='1';
```


```
b1<='1';
```

```
wait;
```

```
end process;
```

```
end Dataflow;
```

TBW Waveform

 


XOR Gate Behavioral Model

VHD Code:

```
entity XOR_GATE_BV is
    Port ( A : in STD_LOGIC;
           B : in STD_LOGIC;
           C : out STD_LOGIC);
end XOR_GATE_BV;

architecture Behavioral of XOR_GATE_BV is
begin
    process(A,B)
    begin
        if(A=B) then
            C<='0';
        else
            C<='1';
        end if;
    end process;
end Behavioral;
```

RTL Diagram

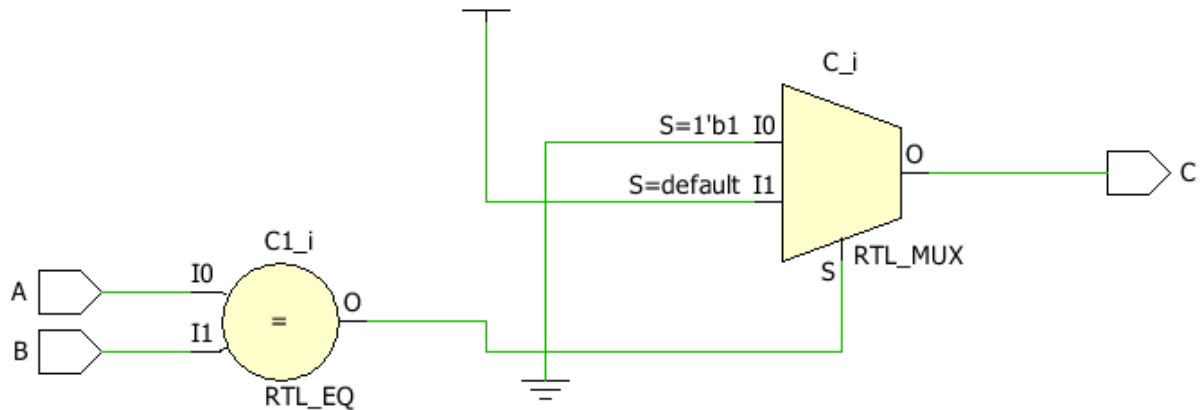

TBW Code:

entity XOR_GATE_TBW is

-- Port ();

end XOR_GATE_TBW;

architecture Behavioral of XOR_GATE_TBW is

component XOR_GATE_BV is

Port (A : in STD_LOGIC;

B: in STD_LOGIC;

C : out STD_LOGIC);

end component;

Signal a1:STD_LOGIC:= '0';

Signal b1:STD_LOGIC:= '0';

Signal c1:STD_LOGIC;

begin

UUT: XOR_GATE_BV Port map(A=>a1, B=>b1, C=>c1);


stim_proc: process

```

begin
wait for 100ns;
a1<='0';
b1<='0';
wait for 100ns;
a1<='0';
b1<='1';
wait for 100ns;
a1<='1';
b1<='0';
wait for 100ns;
a1<='1';
b1<='1';
wait;
end process;
end Behavioral;

```

TBW Waveform

 

XNOR Gate Dataflow Model

VHD Code:

entity XNOR_DF is

```
Port ( a : in STD_LOGIC;  
      b : in STD_LOGIC;  
      c : out STD_LOGIC);
```

end XNOR_DF;


architecture Dataflow of XNOR_DF is

begin

```
c<=a XNOR b;
```

end Dataflow;

RTL Diagram

 

TBW Code:

```


entity XNOR_DF_TBW is
-- Port ( );
end XNOR_DF_TBW;
architecture Dataflow of XNOR_DF_TBW is
component XNOR_DF is
    Port ( a : in STD_LOGIC;
           b : in STD_LOGIC;
           c : out STD_LOGIC);
end component;
Signal a1:STD_LOGIC:='0';
Signal b1:STD_LOGIC:='0';
Signal c1:STD_LOGIC;
begin
UUT: XNOR_DF Port map(a=>a1, b=>b1, c=>c1);
stim_proc: process
begin
wait for 100ns;
a1<='0';
b1<='0';
wait for 100ns;
a1<='0';
b1<='1';
wait for 100ns;

a1<='1';
b1<='0';

```

```
wait for 100ns;  
a1<='1';  
b1<='1';  
wait;  
end process;  
end Dataflow;
```

TBW Waveform

 


XNOR Gate Behavioral Model

VHD Code:

```
entity XNOR_GATE_BV is
    Port ( A : in STD_LOGIC;
           B : in STD_LOGIC;
           C : out STD_LOGIC);
end XNOR_GATE_BV;

architecture Behavioral of XNOR_GATE_BV is
begin
    process(A,B)
    begin
        if(A=B) then
            C<='1';
        else
            C<='0';
        end if;
    end process;
end Behavioral;
```

RTL Diagram

 

TBW Code:

entity XNOR_GATE_TBW is

-- Port ();

end XNOR_GATE_TBW;

architecture Behavioral of XNOR_GATE_TBW is

component XNOR_GATE_BV is

Port (A : in STD_LOGIC;

B : in STD_LOGIC;

C : out STD_LOGIC);

end component;

Signal a1:STD_LOGIC:='0';

Signal b1:STD_LOGIC:='0';

Signal c1:STD_LOGIC;

begin

UUT: XNOR_GATE_BV Port map(A=>a1, B=>b1, C=>c1);


stim_proc: process

```

begin
wait for 100ns;
a1<='0';
b1<='0';
wait for 100ns;
a1<='0';
b1<='1';
wait for 100ns;
a1<='1';
b1<='0';
wait for 100ns;
a1<='1';
b1<='1';
wait;
end process;
end Behavioral;

```

TBW Waveform

 

AND_NAND Gate Dataflow Model

VHD Code:

entity AND_NAND_DF is

Port (A : in STD_LOGIC;

B : in STD_LOGIC;

C : out STD_LOGIC);

end AND_NAND_DF;


architecture Dataflow of AND_NAND_DF is

begin

C<=(A NAND B) NAND (A NAND B);

end Dataflow;

RTL Diagram

 

TBW Code:

entity AND_NAND_TBW is

-- Port ();

end AND_NAND_TBW;

architecture Dataflow of AND_NAND_TBW is

component NAND_DF is

```

    Port ( A : in STD_LOGIC;
           B : in STD_LOGIC;
           C : out STD_LOGIC);
end component;

Signal a1:STD_LOGIC:='0';
Signal b1:STD_LOGIC:='0';
Signal c1:STD_LOGIC;

begin


UUT: AND_NAND_DF Port map(A=>a1, B=>b1, C=>c1);

stim_proc: process
begin
wait for 100ns;
a1<='0';
b1<='0';
wait for 100ns;
a1<='0';
b1<='1';
wait for 100ns;
a1<='1';
b1<='0';
wait for 100ns;
a1<='1';
b1<='1';
wait;
end process;

end Dataflow;

```

TBW Waveform

 

OR_NAND Gate Dataflow Model

VHD Code:

entity OR_NAND_DF is

Port (A : in STD_LOGIC;

B : in STD_LOGIC;

C : out STD_LOGIC);

end OR_NAND_DF;


architecture Dataflow of OR_NAND_DF is

begin

C<=((A NAND A) NAND (B NAND B));

end Dataflow;

RTL Diagram

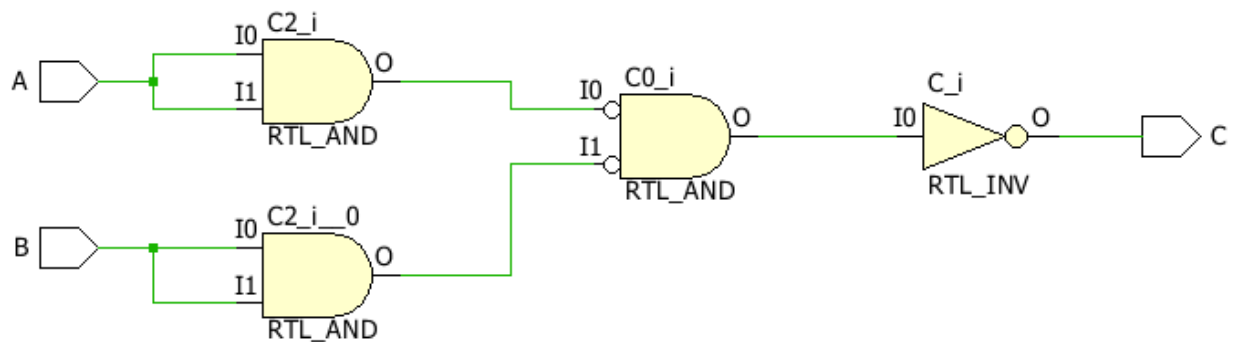

TBW Code:

entity AND_NAND_TBW is

-- Port ();

end AND_NAND_TBW;

architecture Dataflow of AND_NAND_TBW is

```
component NAND_DF is
    Port ( A : in STD_LOGIC;
           B : in STD_LOGIC;
           C : out STD_LOGIC);
end component;


Signal a1:STD_LOGIC:='0';
Signal b1:STD_LOGIC:='0';
Signal c1:STD_LOGIC;

begin
    UUT: AND_NAND_DF Port map(A=>a1, B=>b1, C=>c1);

    stim_proc: process
    begin
        wait for 100ns;
        a1<='0';
        b1<='0';
        wait for 100ns;
        a1<='0';
        b1<='1';
        wait for 100ns;
        a1<='1';
        b1<='0';
        wait for 100ns;
        a1<='1';
        b1<='1';
        wait;
    end process;
```

```
end Dataflow;
```

TBW Waveform

 

NOT_NAND Gate Dataflow Model

VHD Code:

```
entity NOT_NAND_DF is
```

```
    Port ( A : in STD_LOGIC;
```

```
          B : out STD_LOGIC);
```



```

end NOT_NAND_DF;

architecture Dataflow of NOT_NAND_DF is

begin

B<=(A NAND A);

end Dataflow;

```

RTL Diagram



TBW Code:

```

entity NOT_NAND_TBW is
-- Port ( );
end NOT_NAND_TBW;

architecture Dataflow of NOT_NAND_TBW is

component NOT_NAND_DF is
    Port ( A : in STD_LOGIC;
          B : out STD_LOGIC);
end component;

Signal a1:STD_LOGIC:='0';
Signal b1:STD_LOGIC;

begin

```


```

UUT: NOT_NAND_DF Port map(A=>a1, B=>b1);

stim_proc: process
begin
wait for 100ns;
a1<='0';
wait for 100ns;
a1<='1';
wait;
end process;
end Dataflow;

```

TBW Waveform

 

XOR_NAND Gate Dataflow Model

VHD Code:

```

entity XOR_NAND_DF is
  Port ( A : in STD_LOGIC;
        B : in STD_LOGIC;

```

```

        C : out STD_LOGIC);
end XOR_NAND_DF;

```

architecture Dataflow of XOR_NAND_DF is

```
begin
```


```

C<=((A NAND A) NAND B) NAND (A NAND (B NAND B));

```

```
end Dataflow;
```

RTL Diagram

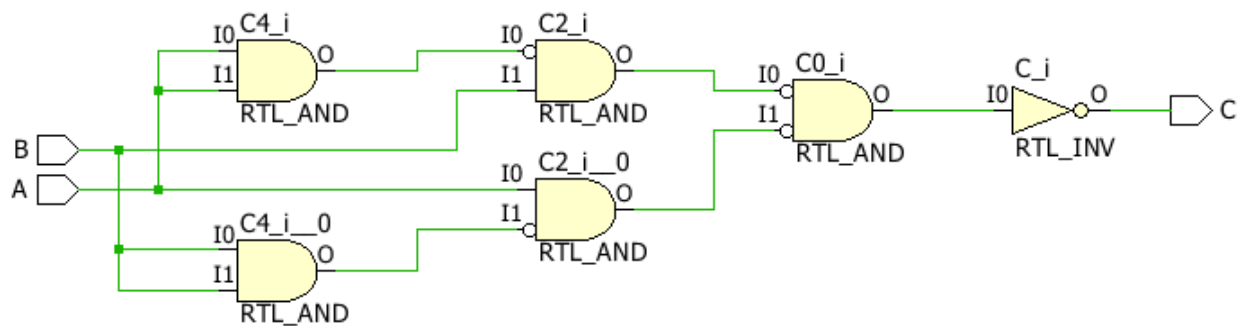

TBW Code:

```
entity XOR_NAND_TBW is
```

```
-- Port ( );
```

```
end XOR_NAND_TBW;
```

architecture Dataflow of XOR_NAND_TBW is

```
component XOR_NAND_DF is
```

```
    Port ( A : in STD_LOGIC;
```

```
        B : in STD_LOGIC;
        C : out STD_LOGIC);
end component;
Signal a1:STD_LOGIC:='0';
Signal b1:STD_LOGIC:='0';
Signal c1:STD_LOGIC;
begin
UUT: XOR_NAND_DF Port map(A=>a1, B=>b1, C=>c1);
stim_proc: process
begin
wait for 100ns;
a1<='0';
b1<='0';
wait for 100ns;

a1<='0';
b1<='1';


wait for 100ns;

a1<='1';
b1<='0';

wait for 100ns;
a1<='1';
b1<='1';
```

```
wait;  
end process;  
end Dataflow;
```

TBW Waveform

 

XNOR_NAND Gate Dataflow Model

VHD Code:

```
entity XNOR_NAND_DF is  
    Port ( A : in STD_LOGIC;  
           B : in STD_LOGIC;
```

```

        C : out STD_LOGIC);
end XNOR_NAND_DF;

```

architecture Dataflow of XNOR_NAND_DF is

```
begin
```


```

C<=((A NAND A) NAND B) NAND (A NAND (B NAND B)) NAND ((A NAND A) NAND
B) NAND (A NAND (B NAND B));

```

```
end Dataflow;
```

RTL Diagram

 

TBW Code:

```
entity XNOR_NAND_TBW is
```

```
-- Port ( );
```

```
end XNOR_NAND_TBW;
```

architecture Dataflow of XNOR_NAND_TBW is

```
component XNOR_NAND_DF is
```

```
Port ( A : in STD_LOGIC;
```

```
      B : in STD_LOGIC;
```

```

        C : out STD_LOGIC);
end component;
Signal a1:STD_LOGIC:='0';
Signal b1:STD_LOGIC:='0';
Signal c1:STD_LOGIC;
begin
UUT: XNOR_NAND_DF Port map(A=>a1, B=>b1, C=>c1);
stim_proc: process
begin
wait for 100ns;
a1<='0';
b1<='0';
wait for 100ns;

a1<='0';
b1<='1';

wait for 100ns;


a1<='1';
b1<='0';

wait for 100ns;
a1<='1';
b1<='1';
wait;

```

```
end process;  
end Dataflow;
```

TBW Waveform

 

AND_NOR Gate Dataflow Model

VHD Code:

```
entity AND_NOR_DF is  
    Port ( A : in STD_LOGIC;  
          B : in STD_LOGIC;  
          C : out STD_LOGIC);  
end AND_NOR_DF;
```

 

architecture Dataflow of AND_NOR_DF is

begin

C<=((A NOR A) NOR (B NOR B));

end Dataflow;

RTL Diagram



TBW Code:

entity AND_NOR_TBW is

-- Port ();

end AND_NOR_TBW;

architecture Dataflow of AND_NOR_TBW is

component AND_NOR_DF is

Port (A : in STD_LOGIC;

B : in STD_LOGIC;

C : out STD_LOGIC);

end component;

Signal a1:STD_LOGIC:='0';

```
Signal b1:STD_LOGIC:='0';
Signal c1:STD_LOGIC;
begin
UUT: AND_NOR_DF Port map(A=>a1, B=>b1, C=>c1);
stim_proc: process
begin
wait for 100ns;
a1<='0';
b1<='0';
wait for 100ns;


a1<='0';
b1<='1';

wait for 100ns;

a1<='1';
b1<='0';

wait for 100ns;
a1<='1';
b1<='1';
wait;
end process;
end Dataflow;
```

TBW Waveform

 

OR_NOR Gate Dataflow Model

VHD Code:

entity OR_NOR_DF is

Port (A : in STD_LOGIC;

B : in STD_LOGIC;

C : out STD_LOGIC);

end OR_NOR_DF;


architecture Dataflow of OR_NOR_DF is

```

begin
C<=(A NOR B) NOR (A NOR B);
end Dataflow;

```

RTL Diagram

 

TBW Code:

```

entity OR_NOR_TBW is
-- Port ( );
end OR_NOR_TBW;

architecture Dataflow of OR_NOR_TBW is
component OR_NOR_DF is
    Port ( A : in STD_LOGIC;
           B : in STD_LOGIC;
           C : out STD_LOGIC);
end component;

Signal a1:STD_LOGIC:='0';
Signal b1:STD_LOGIC:='0';

```

```
Signal c1:STD_LOGIC;

begin

UUT: OR_NOR_DF Port map(A=>a1, B=>b1, C=>c1);

stim_proc: process

begin

wait for 100ns;

a1<='0';

b1<='0';

wait for 100ns;


a1<='0';

b1<='1';


wait for 100ns;


a1<='1';

b1<='0';


wait for 100ns;

a1<='1';


b1<='1';

wait;

end process;

end Dataflow;
```

TBW Waveform

 


NOT_NAND Gate Dataflow Model

VHD Code:

```
entity NOT_NOR_DF is
    Port ( A : in STD_LOGIC;
           B : out STD_LOGIC);
end NOT_NOR_DF;

architecture Dataflow of NOT_NOR_DF is
begin
    B<=(A NOR A);
end Dataflow;
```

RTL Diagram

 

TBW Code:

entity NOT_NOR_TBW is

-- Port ();

end NOT_NOR_TBW;

architecture Dataflow of NOT_NOR_TBW is

component NOT_NOR_DF is

Port (A : in STD_LOGIC;

B : out STD_LOGIC);

end component;

Signal a1:STD_LOGIC:='0';

Signal b1:STD_LOGIC;

begin

UUT: NOT_NOR_DF Port map(A=>a1, B=>b1);

stim_proc: process

begin

wait for 100ns;

a1<='0';


wait for 100ns;

```

a1<='1';
wait;
end process;
end Dataflow;

```

TBW Waveform

 

XOR_NOR Gate Dataflow Model

VHD Code:

```

entity XOR_NOR_DF is
    Port ( A : in STD_LOGIC;
           B : in STD_LOGIC;
           C : out STD_LOGIC);
end XOR_NOR _DF;

architecture Dataflow of XOR_NOR _DF is

begin


```



```
C<=((A NOR A) NOR B) NOR (A NOR (B NOR B)) NOR ((A NOR A) NOR B) NOR (A
NOR (B NOR B));
```

```
end Dataflow;
```

RTL Diagram

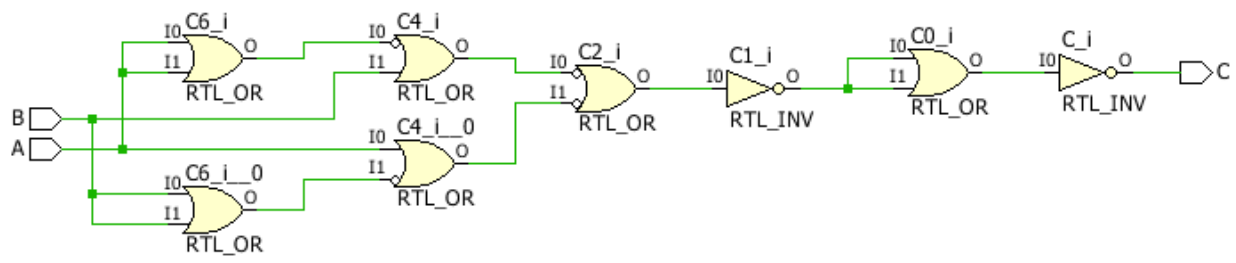

TBW Code:

```
entity XOR_NOR_TBW is
```

```
-- Port ( );
```

```
end XOR_NOR_TBW;
```

```
architecture Dataflow of XOR_NOR_TBW is
```

```
component XOR_NOR_DF is
```

```
Port ( A : in STD_LOGIC;
```

```
      B : in STD_LOGIC;
```

```
      C : out STD_LOGIC);
```

```
end component;
```

```
Signal a1:STD_LOGIC:= '0';
```

```
Signal b1:STD_LOGIC:= '0';
```

```
Signal c1:STD_LOGIC;

begin

UUT: XOR_NOR _DF Port map(A=>a1, B=>b1, C=>c1);

stim_proc: process

begin

wait for 100ns;

a1<='0';

b1<='0';

wait for 100ns;


a1<='0';

b1<='1';


wait for 100ns;


a1<='1';

b1<='0';


wait for 100ns;

a1<='1';


b1<='1';

wait;

end process;

end Dataflow;
```

TBW Waveform

 


XNOR_NOR Gate Dataflow Model

VHD Code:

```
entity XNOR_NOR_DF is
    Port ( A : in STD_LOGIC;
          B : in STD_LOGIC;
          C : out STD_LOGIC);
end XNOR_NOR_DF;

architecture Dataflow of XNOR_NOR_DF is
begin
    C<=((A NOR A) NOR B) NOR (A NOR (B NOR B));
end Dataflow;
```

RTL Diagram

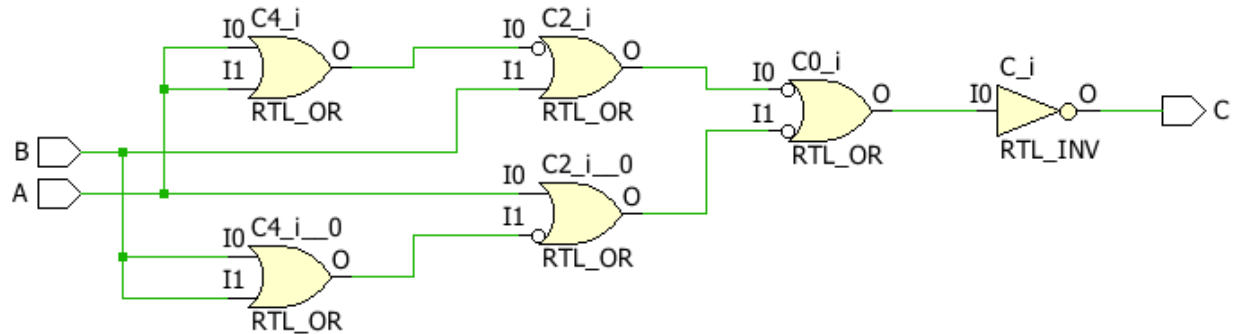

TBW Code:

entity XNOR_NOR_TBW is

-- Port ();

end XNOR_NOR_TBW;

architecture Dataflow of XNOR_NOR_TBW is

component XNOR_NOR_DF is

Port (A : in STD_LOGIC;

B : in STD_LOGIC;

C : out STD_LOGIC);

end component;

Signal a1:STD_LOGIC:='0';

Signal b1:STD_LOGIC:='0';

Signal c1:STD_LOGIC;

begin

```
UUT: XNOR_NOR_DF Port map(A=>a1, B=>b1, C=>c1);
```

```
stim_proc: process
```

```
begin
```

```
wait for 100ns;
```

```
a1<='0';
```

```
b1<='0';
```

```
wait for 100ns;
```

```
a1<='0';
```

```
b1<='1';
```

```
wait for 100ns;
```

```
a1<='1';
```

```
b1<='0';
```

```
wait for 100ns;
```

```
a1<='1';
```


```
b1<='1';
```

```
wait;
```

```
end process;
```

```
end Dataflow;
```

TBW Waveform

 

HALF ADDER Dataflow Model


VHD Code:

```
entity HALF_ADDER_DF is
    Port ( A : in STD_LOGIC;
          B : in STD_LOGIC;
          S : out STD_LOGIC;
          C : out STD_LOGIC);
end HALF_ADDER_DF;

architecture Dataflow of HALF_ADDER_DF is
begin
    S<=A xor B;
    C<=A and B;
```

end Dataflow;

RTL Diagram

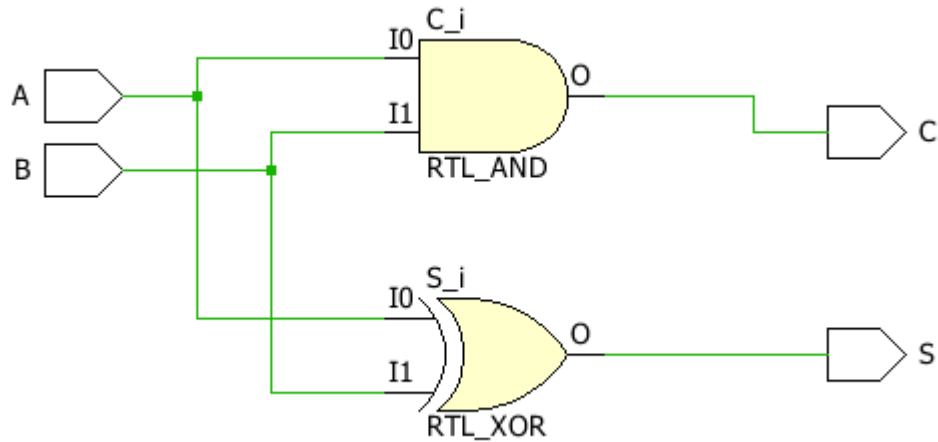

TBW Code:

```
entity HALF_ADDER_TBW is
```

```
-- Port ( );
```

```
end HALF_ADDER_TBW;
```

```
architecture Behavioral of HALF_ADDER_TBW is
```

```
component HALF_ADDER_BV is
```

```
    Port ( A : in STD_LOGIC;
```

```
          B: in STD_LOGIC;
```

```
          S: out STD_LOGIC;
```

```
          C : out STD_LOGIC);
```

```
end component;
```

```
Signal a1:STD_LOGIC:= '0';
```

```
Signal b1:STD_LOGIC:= '0';
```


```
Signal s1:STD_LOGIC;
Signal c1:STD_LOGIC;

begin

UUT: HALF_ADDER_BV Port map(A=>a1, B=>b1, S=>s1, C=>c1);

stim_proc: process
begin
wait for 100ns;
a1<='0';
b1<='0';
wait for 100ns;
a1<='0';
b1<='1';
wait for 100ns;
a1<='1';
b1<='0';
wait for 100ns;
a1<='1';
b1<='1';
wait;
end process;
end Behavioral;
```

TBW Waveform

 

HALF ADDER Behavioral Model

VHD Code:

```
entity HALF_ADDER_BV is
    Port ( A : in STD_LOGIC;
           B : in STD_LOGIC;
           S : out STD_LOGIC;
           C : out STD_LOGIC);
end HALF_ADDER_BV;

architecture Behavioral of HALF_ADDER_BV is
begin
    process(A,B)
    begin
        if(A=B) then
```


```

        S<='0';
    else
        S<='1';
    end if;

    if(A='1' and B='1') then
        C<='1';
    else
        C<='0';
    end if;
end process; end Behavioral;

```

RTL Diagram

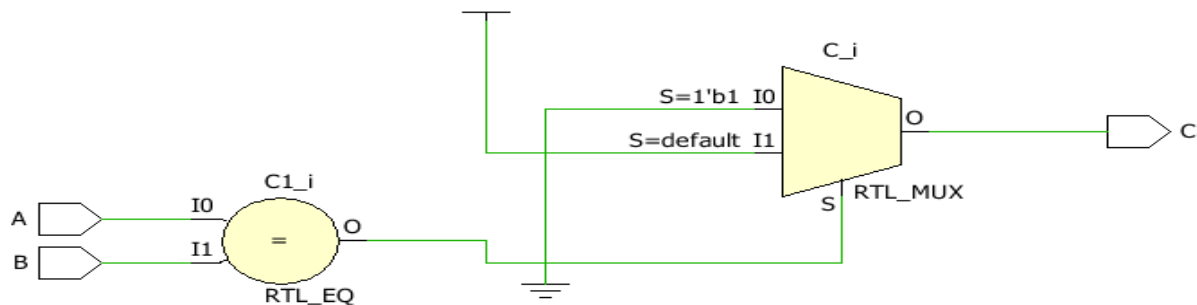

TBW Code:

```

entity HALF_ADDER_TBW is
-- Port ( );
end HALF_ADDER_TBW;

architecture Behavioral of HALF_ADDER_TBW is
component HALF_ADDER_BV is
    Port ( A : in STD_LOGIC;

```


```

        B: in STD_LOGIC;
        S: out STD_LOGIC;
        C : out STD_LOGIC);
end component;
Signal a1:STD_LOGIC:='0';
Signal b1:STD_LOGIC:='0';
Signal s1:STD_LOGIC;
Signal c1:STD_LOGIC;
begin
UUT: HALF_ADDER_BV Port map(A=>a1, B=>b1, S=>s1, C=>c1);
stim_proc: process
begin
wait for 100ns;
a1<='0';
b1<='0';
wait for 100ns;
a1<='0';
b1<='1';
wait for 100ns;
a1<='1';
b1<='0';
wait for 100ns;
a1<='1';
b1<='1';
wait;
end process;

```

end Behavioral;

TBW Waveform

 

HALF ADDER Structural Model

VHD Code:

entity HALF_ADDER_structural is

Port (x : in STD_LOGIC;

y : in STD_LOGIC;

sum : out STD_LOGIC;

carry : out STD_LOGIC);

end HALF_ADDER_structural;

architecture Structural of HALF_ADDER_structural is

component XOR_DF is

Port (A : in STD_LOGIC;

B : in STD_LOGIC;

C : out STD_LOGIC);

end component;

component AND_DF is

Port (A : in STD_LOGIC;

B : in STD_LOGIC;

C : out STD_LOGIC);

end component;


begin

I1:XOR_DF port map(x,y,sum);

I2:AND_DF port map(x,y,carry);

end Structural;

RTL Diagram

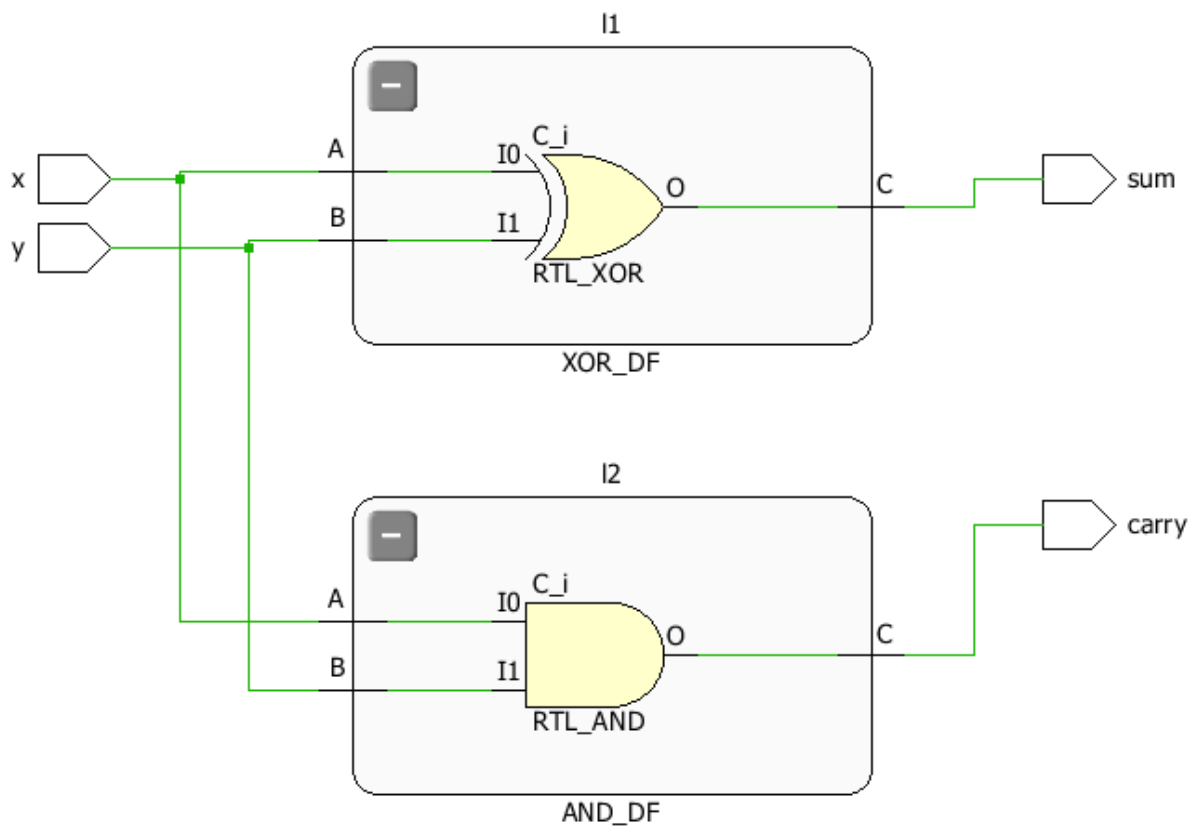

TBW Code:

entity HALF_ADDER_structural is

```
    Port ( x : in STD_LOGIC;  
          y : in STD_LOGIC;  
          sum : out STD_LOGIC;  
          carry : out STD_LOGIC);
```

end HALF_ADDER_structural;

architecture Structural of HALF_ADDER_structural is

component XOR_DF is

```
    Port ( A : in STD_LOGIC;  
          B : in STD_LOGIC;  
          C : out STD_LOGIC);
```

end component;

component AND_DF is

```
    Port ( A : in STD_LOGIC;  
          B : in STD_LOGIC;  
          C : out STD_LOGIC);
```

end component;


begin

l1:XOR_DF port map(x,y,sum);

l2:AND_DF port map(x,y,carry);

end Structural;

TBW Waveform

 

FULL ADDER Dataflow Model

VHD Code:


```

entity FULL_ADDER_DF is
    Port ( A : in STD_LOGIC;
           B : in STD_LOGIC;
           Cin : in STD_LOGIC;
           S : out STD_LOGIC;
           Cout : out STD_LOGIC);
end FULL_ADDER_DF;

architecture Behavioral of FULL_ADDER_DF is
begin
    S<=(A xor B) xor Cin;
    Cout<=(A and B) or (B and Cin) or (Cin and A);
end Behavioral;

```

RTL Diagram

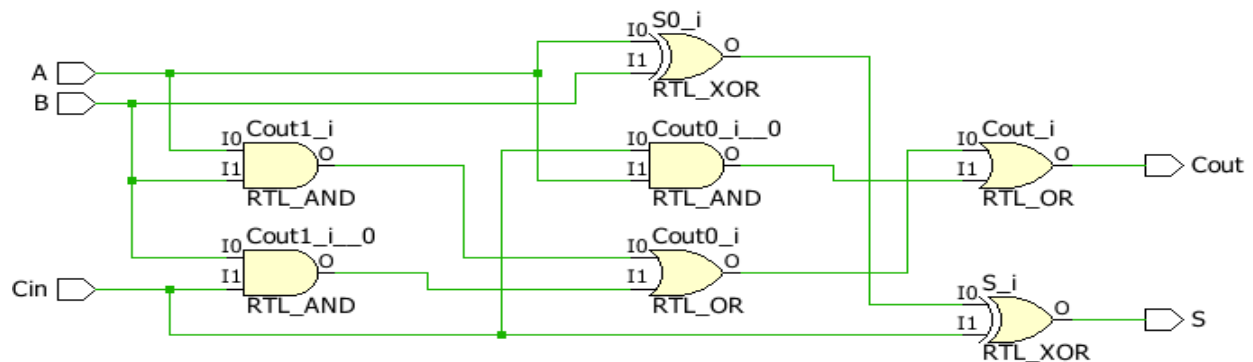

TBW Code:

entity FULL_ADDER_TBW is

-- Port ();

end FULL_ADDER_TBW;

architecture Behavioral of FULL_ADDER_TBW is

component FULL_ADDER_BV is

Port (A : in STD_LOGIC;

B: in STD_LOGIC;

S: out STD_LOGIC;

C : out STD_LOGIC);

end component;

Signal a1:STD_LOGIC:='0';

Signal b1:STD_LOGIC:='0';

Signal s1:STD_LOGIC;


Signal c1:STD_LOGIC;

begin

UUT: FULL_ADDER_BV Port map(A=>a1, B=>b1, S=>s1, C=>c1);


```
stim_proc: process
begin
wait for 100ns;
a1<='0';
b1<='0';
wait for 100ns;
a1<='0';
b1<='1';
wait for 100ns;
a1<='1';
b1<='0';
wait for 100ns;
a1<='1';
b1<='1';
wait;
end process;
end Behavioral;
```

TBW Waveform

 

FULL ADDER Behavioral Model

VHD Code:

```
entity FULL_ADDER_BV is
    Port ( A : in STD_LOGIC;
          B : in STD_LOGIC;
          Cin: in STD_LOGIC;
          S : out STD_LOGIC;
          Cout : out STD_LOGIC);
end FULL_ADDER_BV;
```

architecture Behavioral of FULL_ADDER_BV is

begin

process(A,B,Cin)

begin

if((A='0') and (B=Cin)) then

S<='0';

else

S<='1';

end if;

if((A='1') and (B=Cin)) then

S<='1';

else

S<='0';

end if;

if((A='0') and (B='1' and Cin='1')) then

Cout<='1';

else

Cout<='0';

end if;

if((A='1') and (B='0' and Cin='0')) then

Cout<='0';

else


Cout<='1';

end if;

end process;

end Behavioral;

RTL Diagram

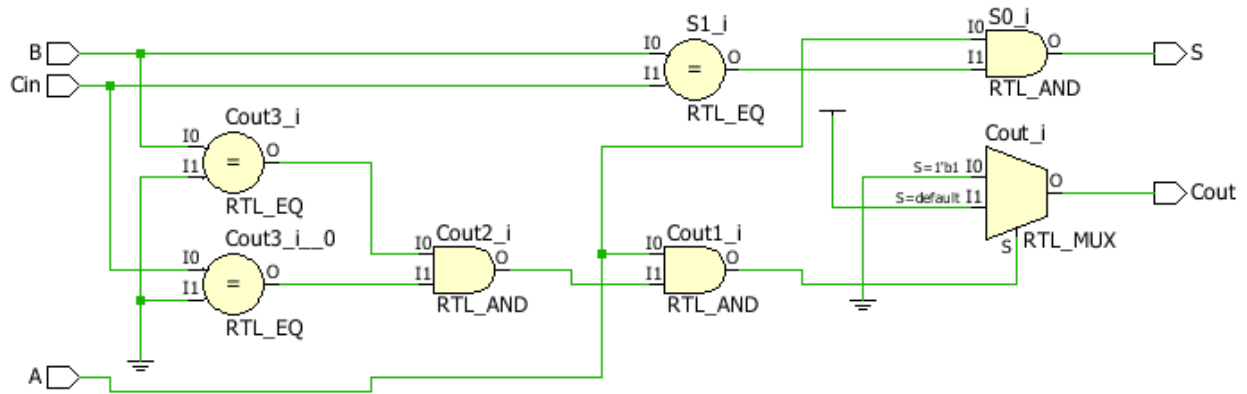

TBW Code:

entity FULL_ADDER_TBW is

-- Port ();

end FULL_ADDER_TBW;

architecture Behavioral of FULL_ADDER_TBW is

component FULL_ADDER_BV is

Port (A : in STD_LOGIC;

B: in STD_LOGIC;

S: out STD_LOGIC;


C : out STD_LOGIC);

end component;

Signal a1:STD_LOGIC:= '0';

```
Signal b1:STD_LOGIC:='0';
Signal s1:STD_LOGIC;
Signal c1:STD_LOGIC;
begin
UUT: FULL_ADDER_BV Port map(A=>a1, B=>b1, S=>s1, C=>c1);
stim_proc: process
begin
wait for 100ns;
a1<='0';
b1<='0';
wait for 100ns;
a1<='0';
b1<='1';
wait for 100ns;
a1<='1';
b1<='0';
wait for 100ns;
a1<='1';
b1<='1';
wait;
end process;
end Behavioral;
```

TBW Waveform

 

FULL ADDER Structural Model

VHD Code:

entity FULL_ADDER_structural is

Port (x : in STD_LOGIC;

y : in STD_LOGIC;

z : in STD_LOGIC;

sum : out STD_LOGIC;

carry : out STD_LOGIC);

end FULL_ADDER_structural;

architecture Structural of FULL_ADDER_structural is

component HALF_ADDER_DF is

```
Port ( A : in STD_LOGIC;  
      B : in STD_LOGIC;  
      S : out STD_LOGIC;  
      C : out STD_LOGIC);
```

end component;

component OR_DF is

```
Port ( a : in STD_LOGIC;  
      b : in STD_LOGIC;  
      c : out STD_LOGIC);
```

end component;

signal s1:std_logic;

signal c1:std_logic;

signal c2:std_logic;

begin


I1:HALF_ADDER_DF port map(x,y,s1,c1);

I2:HALF_ADDER_DF port map(s1,z,sum,c2);

I3:OR_DF port map(c1,c2,carry);

end Structural;

RTL Diagram

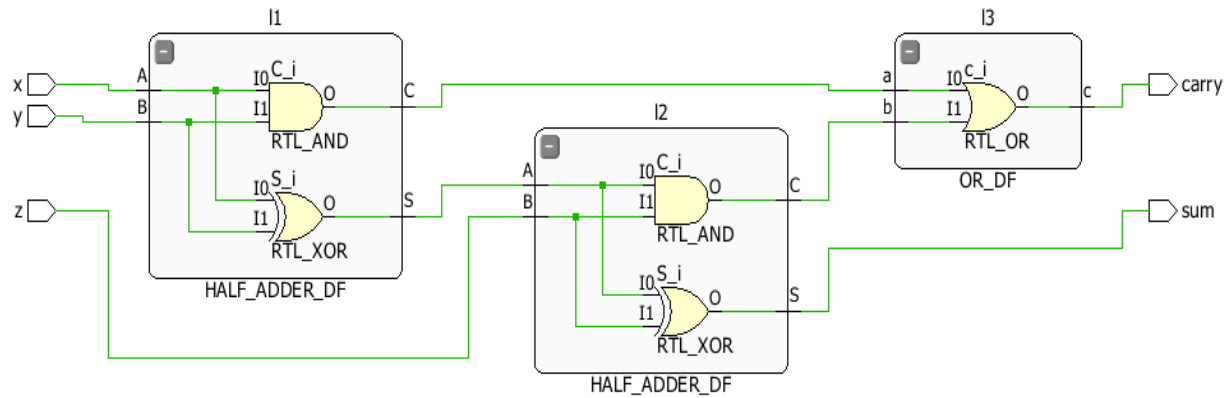

TBW Code:

entity FULL_ADDER_TBW is

-- Port ();

end FULL_ADDER_TBW;

architecture Structural of FULL_ADDER_TBW is

component FULL_ADDER_structural is

Port (x : in STD_LOGIC;

y: in STD_LOGIC;

z: in STD_LOGIC;

sum: out STD_LOGIC;

carry : out STD_LOGIC);

end component;

Signal x1:STD_LOGIC:= '0';

Signal y1:STD_LOGIC:= '0';

Signal z1:STD_LOGIC:= '0';

Signal s1:STD_LOGIC;

Signal c1:STD_LOGIC;

begin


```
UUT: FULL_ADDER_structural Port map(x=>x1, y=>y1, z=>z1, sum=>s1,  
carry=>c1);
```

```
stim_proc: process
```

```
begin
```

```
wait for 50ns;
```

```
x1<='0';
```

```
y1<='0';
```

```
z1<='1';
```

```
wait for 50ns;
```

```
x1<='0';
```

```
y1<='1';
```

```
z1<='0';
```

```
wait for 50ns;
```

```
x1<='0';
```

```
y1<='1';
```

```
z1<='1';
```

```
wait for 50ns;
```

```
x1<='1';
```

```
y1<='0';
```

```
z1<='0';
```

```
wait for 50ns;
```

```
x1<='1';
```

```
y1<='0';
```

```
z1<='1';
```

```
wait for 50ns;
```

```
x1<='1';
```

```
y1<='1';
```

```
z1<='0';
```


```
wait for 50ns;
```

```

x1<='1';
y1<='1';
z1<='1';
wait for 50ns;
end process;
end Structural;

```

TBW Waveform

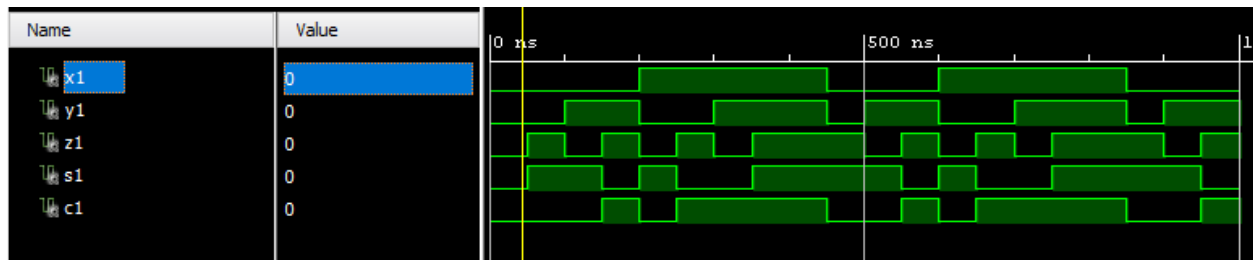

2:1 MUX Dataflow Model


VHD Code:

```

entity MUX_2_1_DF is
  Port ( I0 : in STD_LOGIC;
         I1 : in STD_LOGIC;
         S : in STD_LOGIC;
         Y : out STD_LOGIC);
end MUX_2_1_DF;
architecture Dataflow of MUX_2_1_DF is
begin
  Y<=((NOT S) AND I0) OR (S AND I1);
end Dataflow;

```

RTL Diagram

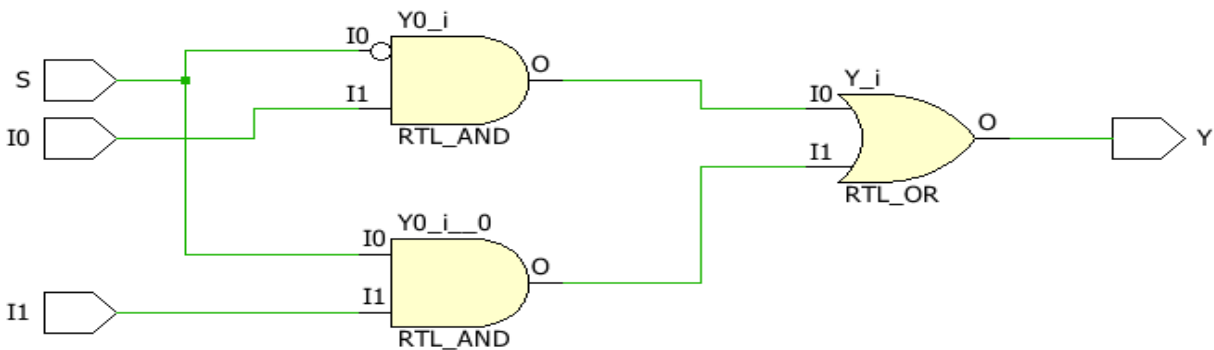

TBW Code:

entity MUX_2_1_TBW is

-- Port ();

end MUX_2_1_TBW;

architecture Dataflow of MUX_2_1_TBW is

component MUX_2_1_BV is

Port (I0 : in STD_LOGIC;

I1 : in STD_LOGIC;

S : in STD_LOGIC;

Y : out STD_LOGIC);

end component;

signal i01: STD_LOGIC:= '0';

signal i11: STD_LOGIC:= '0';

signal s1: STD_LOGIC:= '0';

signal y1: STD_LOGIC;

begin


UUT: MUX_2_1_DF Port map(I0=>i01, I1=>i11, S=>s1, Y=>y1);

```

stim_proc: process
begin
wait for 100ns;
s1<='0';
wait for 100ns;
s1<='1';
wait;
end process;
end Dataflow;

```

TBW Waveform

 

2:1 MUX Behavioral Model

VHD Code:

```

entity MUX_2_1_DF is
  Port ( I0 : in STD_LOGIC;
         I1 : in STD_LOGIC;
         S : in STD_LOGIC;
         Y : out STD_LOGIC);
end MUX_2_1_DF;

```


```

architecture Behavioral of MUX_2_1_DF is

```

```
begin
process(I0,I1,S)
begin
  if(S='0') then
    Y <= I0;
  else
    Y<= I1;
  end if;
end process;
end Behavioral;
```

RTL Diagram

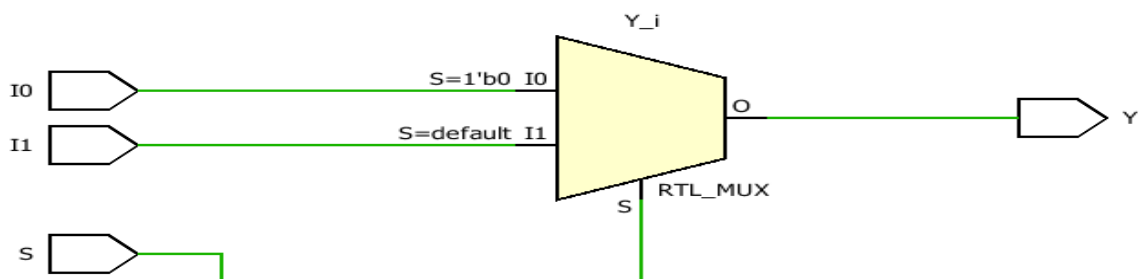

TBW Code:

```
entity MUX_2_1_TBW is
-- Port ( );
end MUX_2_1_TBW;
```

architecture Behavioral of MUX_2_1_TBW is

component MUX_2_1_DF is

Port (I0 : in STD_LOGIC;

I1: in STD_LOGIC;

S: in STD_LOGIC;

Y : out STD_LOGIC);

end component;

Signal i01:STD_LOGIC:='0';

Signal i11:STD_LOGIC:='0';

Signal s1:STD_LOGIC:='0';

Signal y1:STD_LOGIC;

begin

UUT: MUX_2_1_DF Port map(I0=>i01, I1=>i11, S=>s1, Y=>y1);

stim_proc: process

begin

wait for 100ns;


s1<='1';

wait;

end process;

end Behavioral;

TBW Waveform

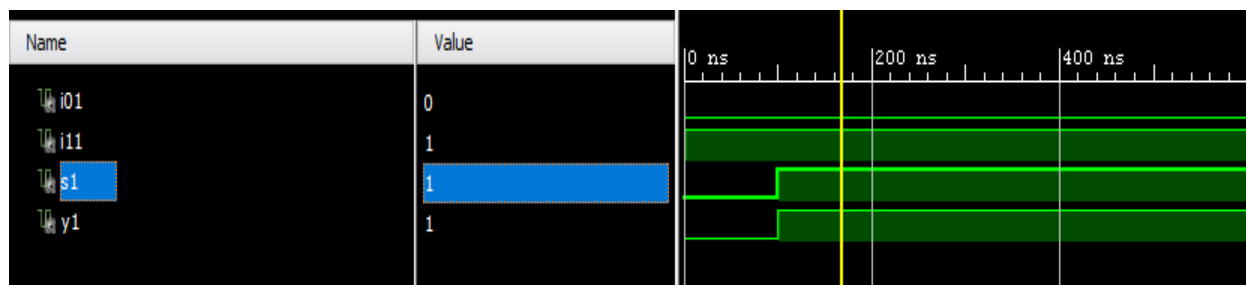


2:1 MUX Dataflow Model

VHD Code:

```
entity MUX_2_1_dataflow is
    Port ( I0 : in STD_LOGIC;
          I1 : in STD_LOGIC;
          S : in STD_LOGIC;
          Y : out STD_LOGIC);
end MUX_2_1_dataflow;

architecture Dataflow of MUX_2_1_dataflow is
begin
    Y <= (((not S) and I0) or (S and I1));
end Dataflow;
```

RTL Diagram

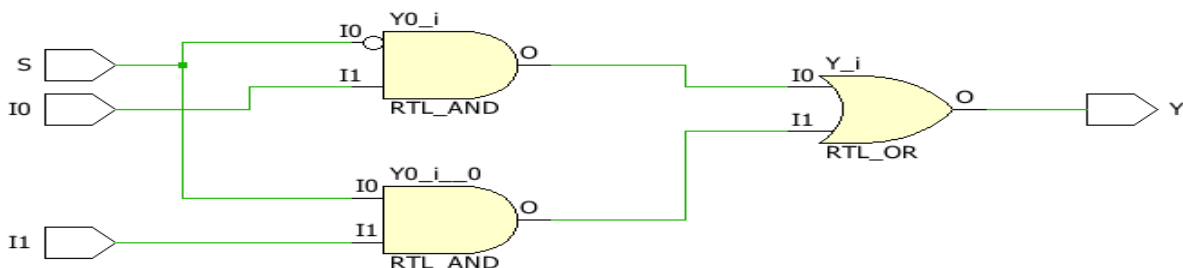

TBW Code:

```
entity MUX_2_1_TBW is
    -- Port ( );
```

```

end MUX_2_1_TBW;

architecture Behavioral of MUX_2_1_TBW is
component MUX_2_1_DF is
    Port ( I0 : in STD_LOGIC;
           I1: in STD_LOGIC;
           S: in STD_LOGIC;
           Y : out STD_LOGIC);
end component;

Signal i01:STD_LOGIC:='0';
Signal i11:STD_LOGIC:='0';
Signal s1:STD_LOGIC:='0';
Signal y1:STD_LOGIC;

begin

UUT: MUX_2_1_DF Port map(I0=>i01, I1=>i11, S=>s1, Y=>y1);

stim_proc: process
begin
wait for 100ns;

s1<='1';


wait;

end process;

end Behavioral;

```

TBW Waveform

 

4:1 MUX Dataflow Model

VHD Code:

```
entity MUX_4_1_DF is
  Port ( IP : in STD_LOGIC_VECTOR (3 downto 0);


        S : in STD_LOGIC_VECTOR (1 downto 0);

        Y : out STD_LOGIC);
end MUX_4_1_DF;

architecture Dataflow of MUX_4_1_DF is
begin
  Y <= IP(0) when S="00" else
        IP(1) when S="01" else
        IP(2) when S="10" else
        IP(3);

end Dataflow;
```

RTL Diagram

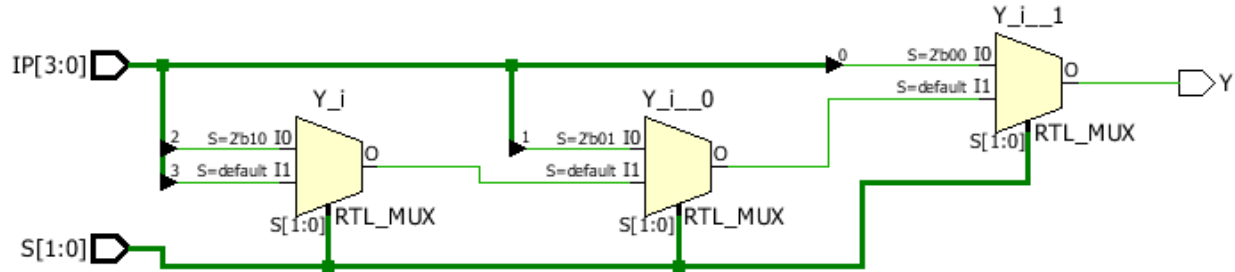

TBW Code:

```
entity MUX_4_1_TBW is
-- Port ( );
end MUX_4_1_TBW;

architecture Behavioral of MUX_4_1_TBW is
component MUX_4_1_BV is
    Port ( IP : in STD_LOGIC_VECTOR (3 downto 0);
          S : in STD_LOGIC_VECTOR (1 downto 0);
          Y : out STD_LOGIC);
end component;

Signal IP:STD_LOGIC_VECTOR(3 downto 0):="1010";
Signal S:STD_LOGIC_VECTOR(1 downto 0):="00";
Signal y1:STD_LOGIC;

begin
    UUT: MUX_4_1_BV Port map(IP=>IP, S=>S, Y=>y1);


    stim_proc: process
    begin
```

```

wait for 100ns;
S(0)<='0';
S(1)<='1';
wait for 100ns;
S(0)<='1';
S(1)<='0';
wait for 100ns;
S(0)<='1';
S(1)<='1';
wait;
end process;
end Behavioral;

```

TBW Waveform

 

4:1 MUX Behavioral Model

VHD Code:

```
entity MUX_4_1_BV is
    Port ( IP : in STD_LOGIC_VECTOR (3 downto 0);
          S : in STD_LOGIC_VECTOR (1 downto 0);
          Y : out STD_LOGIC);
end MUX_4_1_BV;

architecture Behavioral of MUX_4_1_BV is
begin
    process(IP,S)
    begin
        case S is
            when "00" => Y <= IP(0);
            when "01" => Y <= IP(1);
            when "10" => Y <= IP(2);
            when "11" => Y <= IP(3);
```

```

        when others => NULL;


    end case;

end process;

end Behavioral;

```

RTL Diagram

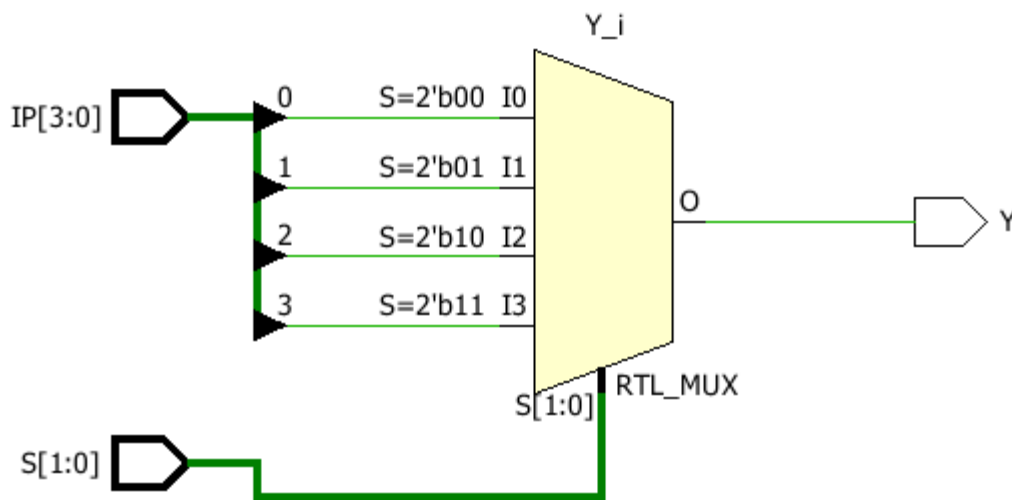

TBW Code:

```

entity MUX_4_1_TBW is
-- Port ( );
end MUX_4_1_TBW;

architecture Behavioral of MUX_4_1_TBW is
component MUX_4_1_BV is
    Port ( IP : in STD_LOGIC_VECTOR (3 downto 0);
          S : in STD_LOGIC_VECTOR (1 downto 0);


```

```

        Y : out STD_LOGIC);
end component;
Signal IP:STD_LOGIC_VECTOR(3 downto 0):="1010";
Signal S:STD_LOGIC_VECTOR(1 downto 0):="00";
Signal y1:STD_LOGIC;
begin
UUT: MUX_4_1_BV Port map(IP=>IP, S=>S, Y=>y1);
stim_proc: process
begin
wait for 100ns;
S(0)<='0';
S(1)<='1';
wait for 100ns;
S(0)<='1';
S(1)<='0';
wait for 100ns;
S(0)<='1';
S(1)<='1';
wait;
end process;
end Behavioral;

```

TBW Waveform

 

3:8 Decoder Dataflow Model

VHD Code:

entity DECODER_3_8_DF is

Port (IP : in STD_LOGIC_VECTOR (2 downto 0);

OP : out STD_LOGIC_VECTOR (7 downto 0));

end DECODER_3_8_DF;

architecture Dataflow of DECODER_3_8_DF is

begin

OP(0) <='1' when IP = "000" else '0';

OP(1) <='1' when IP = "001" else '0';

OP(2) <='1' when IP = "010" else '0';

OP(3) <='1' when IP = "011" else '0';

OP(4) <='1' when IP = "100" else '0';


OP(5) <='1' when IP = "101" else '0';

OP(6) <='1' when IP

OP(7) <='1' when IP

end Dataflow;

RTL

 

Diagram

[illegible]

```
entity DECODER_3_8_TBW is
-- Port ( );
end DECODER_3_8_TBW;

architecture Dataflow of DECODER_3_8_TBW is
component DECODER_3_8_DF is
    Port ( IP : in STD_LOGIC_VECTOR (2 downto 0);
```

```

        OP : out STD_LOGIC_VECTOR (7 downto 0));
end component;
Signal IP:STD_LOGIC_VECTOR(2 downto 0):="000";
Signal OP:STD_LOGIC_VECTOR(7 downto 0);
begin
UUT: DECODER_3_8_DF Port map(IP=>IP, OP=>OP);
stim_proc: process
begin
wait for 100ns;
IP(0)<='0';
IP(1)<='0';
IP(2)<='1';
wait for 100ns;
IP(0)<='0';
IP(1)<='1';
IP(2)<='0';
wait for 100ns;
IP(0)<='0';
IP(1)<='1';
IP(2)<='1';
wait for 100ns;
IP(0)<='1';
IP(1)<='0';
IP(2)<='0';
wait for 100ns;
IP(0)<='1';
IP(1)<='0';
IP(2)<='1';


```

```

wait for 100ns;
IP(0)<='1';
IP(1)<='1';
IP(2)<='0';
wait for 100ns;
IP(0)<='1';
IP(1)<='1';
IP(2)<='1';
wait;
end process;
end Dataflow;

```

TBW Waveform

 

3:8 Decoder Behavioral Model

VHD Code:

entity Decoder_3_8_BV is

Port (IP : in STD_LOGIC_VECTOR (2 downto 0);

OP : out STD_LOGIC_VECTOR (7 downto 0));


```

end Decoder_3_8_BV;

architecture Behavioral of Decoder_3_8_BV is
begin process(IP)
begin
    OP<="00000000";
    case IP is
        when "000" => OP(0) <= '1';
        when "001" => OP(1) <= '1';
        when "010" => OP(2) <= '1';
        when "011" => OP(3) <= '1';
        when "100" => OP(4) <= '1';
        when "101" => OP(5) <= '1';
        when "110" => OP(6) <= '1';
        when "111" => OP(7) <= '1';
        when others => NULL;
    end case;
end process;
end Behavioral;

```

RTL Diagram

 

TBW Code:

```
entity DECODER_3_8_TBW is
-- Port ( );
end DECODER_3_8_TBW;

architecture Dataflow of DECODER_3_8_TBW is
component DECODER_3_8_DF is
    Port ( IP : in STD_LOGIC_VECTOR (2 downto 0);
          OP : out STD_LOGIC_VECTOR (7 downto 0));
end component;

Signal IP:STD_LOGIC_VECTOR(2 downto 0):="000";
Signal OP:STD_LOGIC_VECTOR(7 downto 0);
begin

UUT: DECODER_3_8_DF Port map(IP=>IP, OP=>OP);

stim_proc: process
begin
wait for 100ns;
IP(0)<='0';
IP(1)<='0';
IP(2)<='1';
wait for 100ns;
IP(0)<='0';
IP(1)<='1';
IP(2)<='0';
wait for 100ns;
IP(0)<='0';
IP(1)<='1';
IP(2)<='1';
```

```
wait for 100ns;  
IP(0)<='1';  
IP(1)<='0';  
IP(2)<='0';  
wait for 100ns;  
IP(0)<='1';  
IP(1)<='0';  
IP(2)<='1';  
wait for 100ns;  
IP(0)<='1';  
IP(1)<='1';  
IP(2)<='0';  
wait for 100ns;  
IP(0)<='1';  
IP(1)<='1';  
IP(2)<='1';  
wait;  
end process;  
end Dataflow;
```

TBW Waveform

