



# **HERITAGE INSTITUTE OF TECHNOLOGY**

**Paper Name** - Computer Organisation and Architecture

**Paper Code** - CSE2252

**Team Members** -

Chinki Raj - 2361021

Vivek Kumar - 2361023

Asmita Banerjee - 2361024

Kishalay Kamar - 2361025

Aritra Hutaib - 2361026

# Table of Contents

AND GATE (Dataflow & Behavioral Model)	2
OR GATE (Dataflow & Behavioral Model)	8
NOT GATE (Dataflow & Behavioral Model)	14
NAND GATE (Dataflow & Behavioral Model)	19
NOR GATE (Dataflow & Behavioral Model)	25
XOR GATE (Dataflow & Behavioral Model)	31
XNOR GATE (Dataflow & Behavioral Model)	37
AND GATE using NAND GATE	43
OR GATE using NAND GATE	46
NOT GATE using NAND GATE	49
XOR GATE using NAND GATE	51
XNOR GATE using NAND GATE	54
AND GATE using NOR GATE	57
OR GATE using NOR GATE	60
NOT GATE using NOR GATE	63
XOR GATE using NOR GATE	65
XNOR GATE using NOR GATE	68
HALF ADDER (Dataflow, Behavioral & Structural Model)	71
FULL ADDER (Dataflow, Behavioral & Structural Model)	80
2:1 MUX (Dataflow & Behavioral Model)	91
4:1 MUX (Dataflow & Behavioral Model)	97
3:8 DECODER (Dataflow & Behavioral Model)	103

# AND Gate Dataflow Model

---

## VHD Code:

---


```
entity AND_DF is
  Port ( A : in STD_LOGIC;
        B : in STD_LOGIC;
        C : out STD_LOGIC);
end AND_DF;
architecture Dataflow of AND_DF is
begin

  C <= A AND B;

end Dataflow;
```

## RTL Diagram

---

 

## **TBW Code:**

---

```
entity AND_DF_TBW is
```

```
-- Port ( );
```

```
end AND_DF_TBW;
```

```
architecture Dataflow of AND_DF_TBW is
```

```
component AND_DF is
```

```
    Port ( A : in STD_LOGIC;
```

```
          B : in STD_LOGIC;
```

```
          C : out STD_LOGIC);
```

```
end component;
```

```
Signal a1:STD_LOGIC:='0';
```

```
Signal b1:STD_LOGIC:='0';
```

```
Signal c1:STD_LOGIC;
```

```
begin
```

```
UUT: AND_DF Port map(A=>a1, B=>b1, c=>c1);
```

```
stim_proc: process
```

```
begin
```

```
wait for 100ns;
```

```
a1<='0';
```

```
b1<='0';
```

```
wait for 100ns;
```

```

a1<='0';
b1<='1';

wait for 100ns;

a1<='1';
b1<='0';


wait for 100ns;

a1<='1';
b1<='1';

wait;
end process;
end Dataflow;

```

## TBW Waveform

 

# AND Gate Behavioral Model

---

## VHD Code:

---

```
entity AND_GATE_BV is
```

```
    Port ( A : in STD_LOGIC;
```

```
          B : in STD_LOGIC;
```

```
          C : out STD_LOGIC);
```

```
end AND_GATE_BV;
```

```
architecture Behavioral of AND_GATE_BV is
```

```
begin
```

```
    process(A,B)
```

```
    begin
```

```
        if(A='1' and B='1') then
```

```
            c<='1';
```

```
        else
```

```
            c<='0';
```


```
        end if;
```

```
    end process;
```

```
end Behavioral;
```

## RTL Diagram

---

 

## TBW Code:

---

entity AND\_GATE\_TBW is

-- Port ( );

end AND\_GATE\_TBW;

architecture Behavioral of AND\_GATE\_TBW is

component AND\_GATE\_BV is

Port ( A : in STD\_LOGIC;

B : in STD\_LOGIC;

C : out STD\_LOGIC);

end component;

Signal a1:STD\_LOGIC:='0';

Signal b1:STD\_LOGIC:='0';

Signal c1:STD\_LOGIC;

begin

```
UUT: AND_GATE_BV Port map(A=>a1, B=>b1, C=>c1);
```

```
stim_proc: process
```

```
begin
```

```
wait for 100ns;
```

```
a1<='0';
```

```
b1<='0';
```

```
wait for 100ns;
```

```
a1<='0';
```

```
b1<='1';
```

```
wait for 100ns;
```

```
a1<='1';
```

```
b1<='0';
```

```
wait for 100ns;
```

```
a1<='1';
```


```
b1<='1';
```

```
wait;
```

```
end process;
```

```
end Behavioral;
```

## **TBW Waveform**

 



# OR Gate Dataflow Model

---

## VHD Code:

---

entity OR\_DF is

Port ( a : in STD\_LOGIC;

b : in STD\_LOGIC;

c : out STD\_LOGIC);

end OR\_DF;

architecture Dataflow of OR\_DF is


begin

c <= a OR b;

end Dataflow;

## RTL Diagram

---

 

## **TBW Code:**

---

entity OR\_DF\_TBW is

-- Port ( );

end OR\_DF\_TBW;

architecture Dataflow of OR\_DF\_TBW is

component OR\_DF is

Port ( a : in STD\_LOGIC;

b : in STD\_LOGIC;

c : out STD\_LOGIC);

end component;

Signal a1:STD\_LOGIC:='0';

Signal b1:STD\_LOGIC:='0';

Signal c1:STD\_LOGIC;

begin

UUT: OR\_DF Port map(a=>a1, b=>b1, c=>c1);

stim\_proc: process

begin

wait for 100ns;

a1<='0';


b1<='0';

wait for 100ns;

```
a1<='0';  
b1<='1';  
  
wait for 100ns;  
  
a1<='1';  
b1<='0';  
  
wait for 100ns;  
  
a1<='1';  
b1<='1';  
  
wait;  
end process;  
end Dataflow;
```

## TBW Waveform

---

 

# OR Gate Behavioral Model

---


## VHD Code:

---

```
entity OR_GATE_BV is
    Port ( A : in STD_LOGIC;
           B : in STD_LOGIC;
           C : out STD_LOGIC);
end OR_GATE_BV;

architecture Behavioral of OR_GATE_BV is
begin
    process(A,B)
    begin
        if(A='0' and B='0') then
            c<='0';
        else
            c<='1';
        end if;
    end process;
end Behavioral;
```

## RTL Diagram

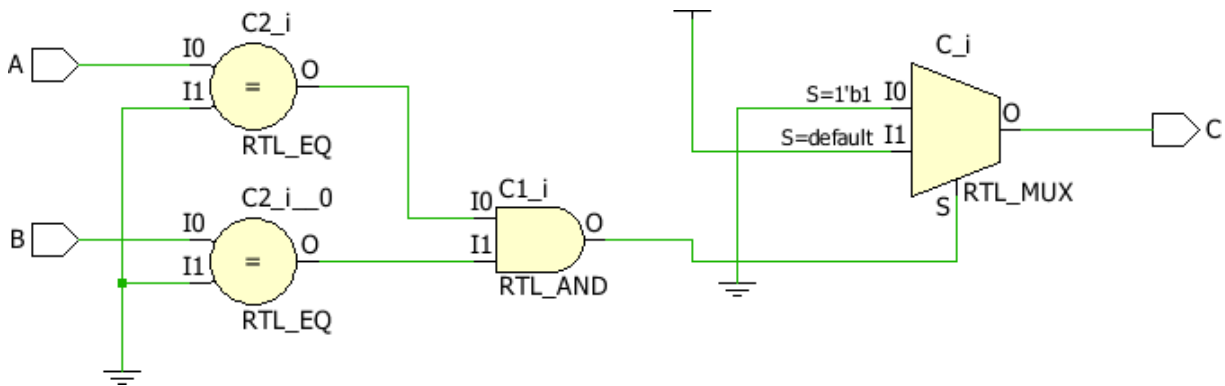

## TBW Code:

entity OR\_GATE\_TBW is

-- Port ( );

end OR\_GATE\_TBW;

architecture Behavioral of OR\_GATE\_TBW is

component OR\_GATE\_BV is

Port ( a : in STD\_LOGIC;

b : in STD\_LOGIC;

c : out STD\_LOGIC);

end component;

Signal a1:STD\_LOGIC:='0';

Signal b1:STD\_LOGIC:='0';

Signal c1:STD\_LOGIC;

begin

```
UUT: OR_GATE_BV Port map(a=>a1, b=>b1, c=>c1);
```

```
stim_proc: process
```

```
begin
```

```
wait for 100ns;
```

```
a1<='0';
```

```
b1<='0';
```

```
wait for 100ns;
```

```
a1<='0';
```

```
b1<='1';
```

```
wait for 100ns;
```

```
a1<='1';
```

```
b1<='0';
```

```
wait for 100ns;
```

```
a1<='1';
```


```
b1<='1';
```

```
wait;
```

```
end process;
```

```
end Behavioral;
```

## TBW Waveform

 

# NOT Gate Dataflow Model

---

## VHD Code:


---

```
entity NOT_DF is
    Port ( a : in STD_LOGIC;
           b : out STD_LOGIC);
end NOT_DF;

architecture Dataflow of NOT_DF is
begin
    b <= NOT a;
end Dataflow;
```

## RTL Diagram

---

 

## TBW Code:

---

```
entity NOT_DF_TBW is
-- Port ( );
```

```

end NOT_DF_TBW;

architecture Dataflow of NOT_DF_TBW is
component NOT_DF is
    Port ( a : in STD_LOGIC;
           b : out STD_LOGIC);
end component;

Signal a1:STD_LOGIC:='0';
Signal b1:STD_LOGIC;

begin

UUT: NOT_DF Port map(a=>a1, b=>b1);

stim_proc: process
begin

wait for 100ns;
a1<='0';

wait for 100ns;
a1<='1';


wait;

end process;

end Dataflow;

```

## TBW Waveform

 



# NOT Gate Behavioral Model

---

## VHD Code:


---

```
entity NOT_GATE_BV is
    Port ( A : in
           STD_LOGIC;
           B : out STD_LOGIC);
end NOT_GATE_BV;

architecture Behavioral of NOT_GATE_BV is
begin
    process(A)
    begin
        if(A='0') then
            B<='1';
        else
            B<='0';
        end if;
    end process;
end Behavioral;
```

## RTL Diagram

---

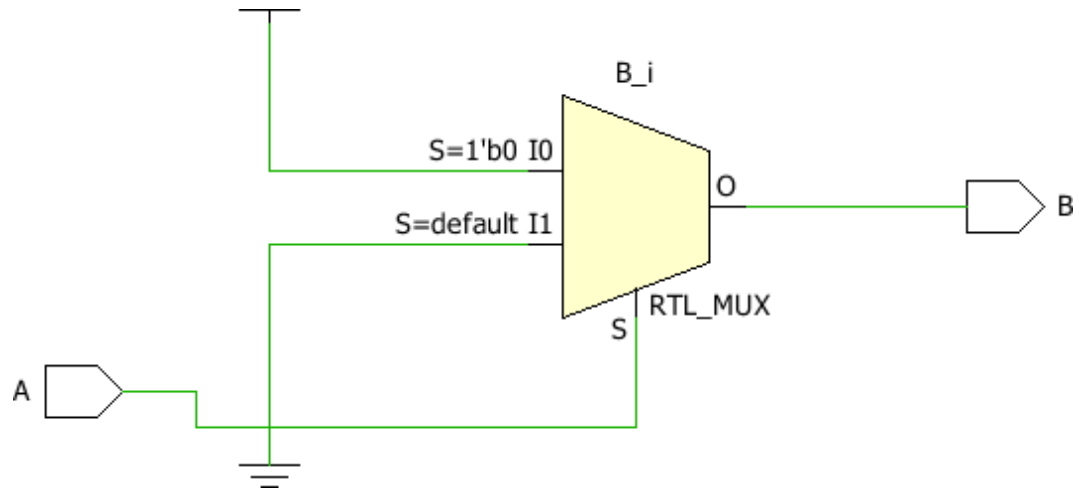

## TBW Code:

---

```
entity NOT_GATE_TBW is
-- Port ( );
end NOT_GATE_TBW;

architecture Behavioral of NOT_GATE_TBW is
component NOT_GATE_BV is
    Port ( a : in STD_LOGIC;
          b : out STD_LOGIC);
end component;


Signal a1:STD_LOGIC:='0';
Signal b1:STD_LOGIC;
```

```

begin
UUT: NOT_GATE_BV Port map(a=>a1, b=>b1);
stim_proc: process
begin
wait for 100ns;
a1<='0';
wait for 100ns;
a1<='1';
wait;
end process;
end Behavioral;

```

## TBW Waveform

 

# NAND Gate Dataflow Model

---

## VHD Code:


---

```
entity NAND_DF is
  Port ( a : in STD_LOGIC;
         b : in STD_LOGIC;
         c : out STD_LOGIC);
end NAND_DF;

architecture Dataflow of NAND_DF is
begin
  c<=a NAND b;
end Dataflow;
```

## RTL Diagram

---

 

## TBW Code:

---

```
entity NAND_DF_TBW is
-- Port ( );
end NAND_DF_TBW;
```

architecture Dataflow of NAND\_DF\_TBW is

component NAND\_DF is

Port ( a : in STD\_LOGIC;

b : in STD\_LOGIC;

c : out STD\_LOGIC);

end component;

Signal a1:STD\_LOGIC:='0';

Signal b1:STD\_LOGIC:='0';

Signal c1:STD\_LOGIC;

begin

UUT: NAND\_DF Port map(a=>a1, b=>b1, c=>c1);

stim\_proc: process

begin

wait for 100ns;

a1<='0';

b1<='0';

wait for 100ns;

a1<='0';

b1<='1';

wait for 100ns;

a1<='1';

b1<='0';

wait for 100ns;

a1<='1';


b1<='1';

wait;

```
end process;  
end Dataflow;
```

## TBW Waveform

---

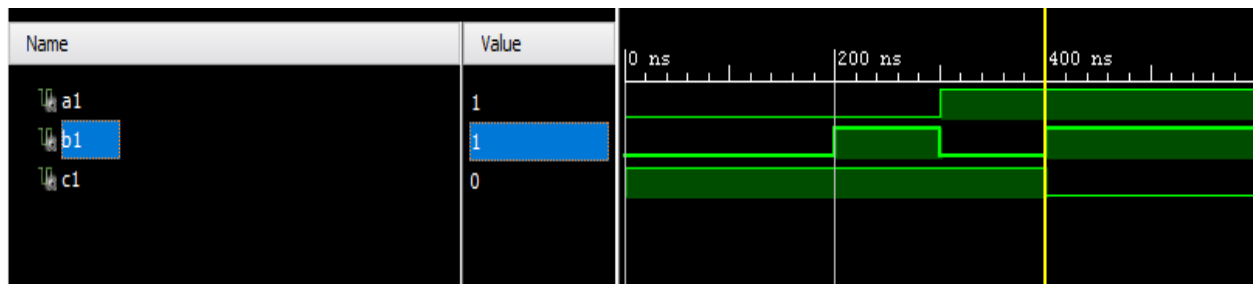

# NAND Gate Behavioral Model

## VHD Code:


---

```
entity NAND_GATE_BV is
    Port ( A : in STD_LOGIC;
           B : in STD_LOGIC;
           C : out STD_LOGIC);
end NAND_GATE_BV;

architecture Behavioral of NAND_GATE_BV is
begin
    process(A,B)
    begin
        if(A='1' and B='1') then
            c<='0';
        else
            c<='1';
        end if;
    end process;
end Behavioral;
```

## RTL Diagram

---

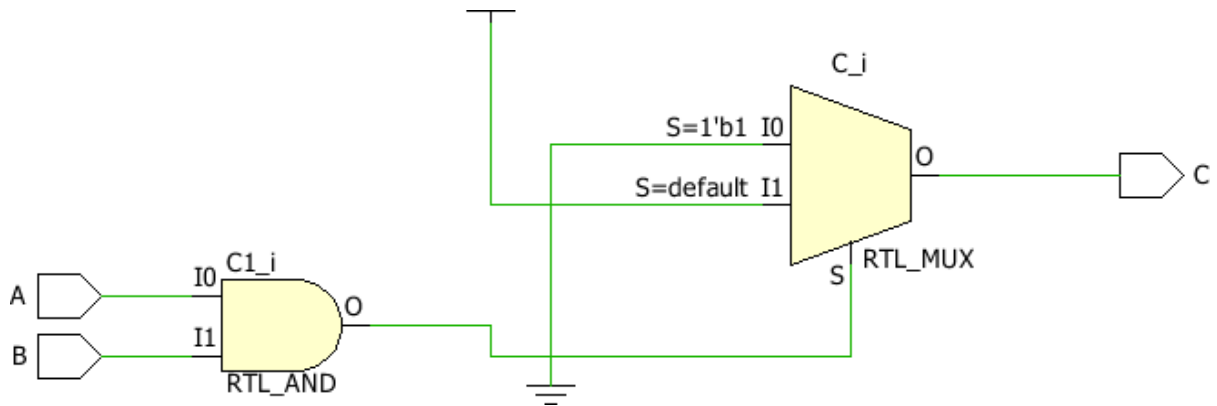

## **TBW Code:**

entity NAND\_GATE\_TBW is

-- Port ( );

end NAND\_GATE\_TBW;

architecture Dataflow of NAND\_GATE\_TBW is

component NAND\_GATE\_BV is

Port ( a : in STD\_LOGIC;

b : in STD\_LOGIC;

c : out STD\_LOGIC);

end component;

Signal a1:STD\_LOGIC:='0';

Signal b1:STD\_LOGIC:='0';

Signal c1:STD\_LOGIC;

begin

UUT: NAND\_GATE\_BV Port map(a=>a1, b=>b1, c=>c1);

stim\_proc: process

begin



```

wait for 100ns;
a1<='0';
b1<='0';

wait for 100ns;
a1<='0';
b1<='1';


wait for 100ns;
a1<='1';
b1<='0';

wait for 100ns;
a1<='1';
b1<='1';

wait;
end process;
end Dataflow;

```

## **TBW Waveform**

 

## **NOR Gate Dataflow Model**

## **VHD Code:**

entity NOR\_DF is

Port ( a : in STD\_LOGIC;

b : in STD\_LOGIC;

c : out STD\_LOGIC);

end NOR\_DF;

architecture Dataflow of NOR\_DF is


begin

c<=a NOR b;

end Dataflow;

## RTL Diagram

---

 

## TBW Code:

---

entity NOR\_DF\_TBW is

-- Port ( );

end NOR\_DF\_TBW;

architecture Dataflow of NOR\_DF\_TBW is

component NOR\_DF is

Port ( a : in STD\_LOGIC;

b : in STD\_LOGIC;

c : out STD\_LOGIC);

end component;

Signal a1:STD\_LOGIC:='0';

Signal b1:STD\_LOGIC:='0';

Signal c1:STD\_LOGIC;

begin

UUT: NOR\_DF Port map(a=>a1, b=>b1, c=>c1);

stim\_proc: process

begin

wait for 100ns;

a1<='0';

b1<='0';

wait for 100ns;

a1<='0';

b1<='1';

wait for 100ns;

a1<='1';

b1<='0';

```
wait for 100ns;
```

```
a1<='1';
```

```
b1<='1';
```


```
wait;
```

```
end process;
```

```
end Dataflow;
```

## **TBW Waveform**

---

 

## **NOR Gate Behavioral Model**

---

### **VHD Code:**

---

```
entity NOR_GATE_BV is
```


```
    Port ( A : in
```

```
    STD_LOGIC;
```

```
B : in STD_LOGIC;
C : out STD_LOGIC);
end NOR_GATE_BV;
architecture Behavioral of NOR_GATE_BV is
begin
process(A,B)
begin
    if(A='0' and B='0') then
        C<='1';
    else
        C<='0';
    end if;
end process;
end Behavioral;
```

## **RTL Diagram**

---

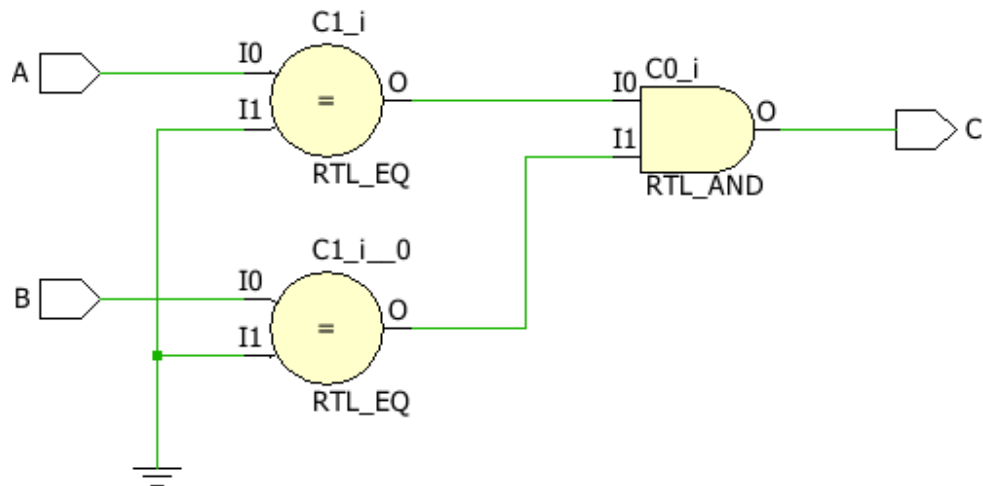

## TBW Code:

---

entity NOR\_GATE\_TBW is

-- Port ( );

end NOR\_GATE\_TBW;

architecture Behavioral of NOR\_GATE\_TBW is

component NOR\_GATE\_BV is

Port ( A : in STD\_LOGIC;

B : in STD\_LOGIC;

C : out STD\_LOGIC);

end component;

Signal a1:STD\_LOGIC:='0';

Signal b1:STD\_LOGIC:='0';

Signal c1:STD\_LOGIC;

begin

UUT: NOR\_GATE\_BV Port map(A=>a1, B=>b1, C=>c1);

stim\_proc: process

```

begin
wait for 100ns;
a1<='0';
b1<='0';

wait for 100ns;
a1<='0';
b1<='1';

wait for 100ns;
a1<='1';
b1<='0';


wait for 100ns;
a1<='1';
b1<='1';

wait;
end process;
end Behavioral;

```

## TBW Waveform

---

 

## XOR Gate Dataflow Model

---

## VHD Code:

entity XOR\_DF is

```
Port ( a : in STD_LOGIC;  
      b : in STD_LOGIC;  
      c : out STD_LOGIC);
```

end XOR\_DF;


architecture Dataflow of XOR\_DF is

begin

```
c<=a XOR b;
```

end Dataflow;

## RTL Diagram

 

## TBW Code:



entity XOR\_DF\_TBW is

-- Port ( );

end XOR\_DF\_TBW;

architecture Dataflow of XOR\_DF\_TBW is

component XOR\_DF is

Port ( a : in STD\_LOGIC;

b : in STD\_LOGIC;

c : out STD\_LOGIC);

end component;

Signal a1:STD\_LOGIC:='0';

Signal b1:STD\_LOGIC:='0';

Signal c1:STD\_LOGIC;

begin

UUT: XOR\_DF Port map(a=>a1, b=>b1, c=>c1);

stim\_proc: process

begin

wait for 100ns;

a1<='0';

b1<='0';

wait for 100ns;

a1<='0';

b1<='1';

```
wait for 100ns;
```

```
a1<='1';
```

```
b1<='0';
```

```
wait for 100ns;
```

```
a1<='1';
```

```
b1<='1';
```


```
wait;
```

```
end process;
```

```
end Dataflow;
```

## TBW Waveform

---

 

## XOR Gate Behavioral Model

---

## **VHD Code:**


---

```
entity XOR_GATE_BV is
    Port ( A : in
           STD_LOGIC;
           B : in STD_LOGIC;
           C : out STD_LOGIC);
end XOR_GATE_BV;

architecture Behavioral of XOR_GATE_BV is
begin
    process(A,B)
    begin
        if(A=B) then
            C<='0';
        else
            C<='1';
        end if;
    end process;
end Behavioral;
```

## **RTL Diagram**

---

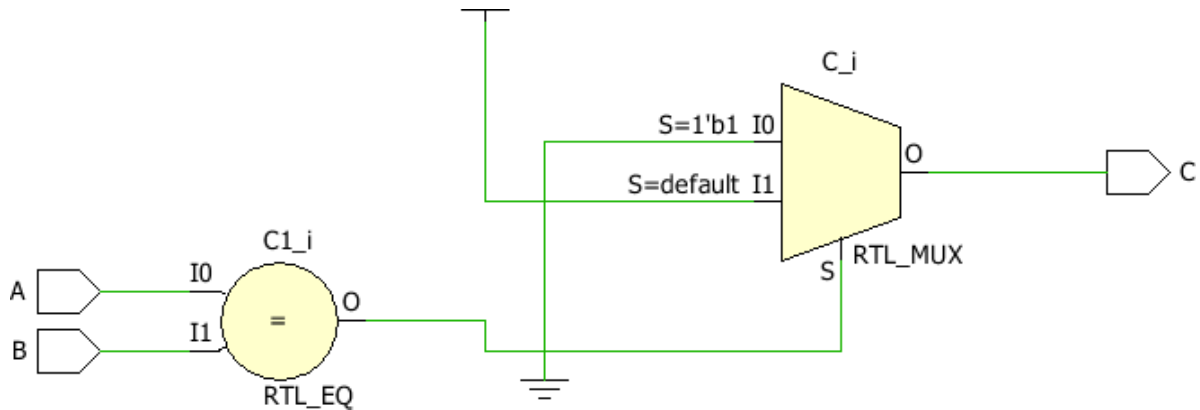

## **TBW Code:**

entity XOR\_GATE\_TBW is

-- Port ( );

end XOR\_GATE\_TBW;

architecture Behavioral of XOR\_GATE\_TBW is

component XOR\_GATE\_BV is

Port ( A : in STD\_LOGIC;

B: in STD\_LOGIC;

C : out STD\_LOGIC);

end component;

Signal a1:STD\_LOGIC:='0';

Signal b1:STD\_LOGIC:='0';

Signal c1:STD\_LOGIC;

begin

UUT: XOR\_GATE\_BV Port map(A=>a1, B=>b1, C=>c1);

stim\_proc: process

```

begin
wait for 100ns;
a1<='0';
b1<='0';

wait for 100ns;
a1<='0';
b1<='1';

wait for 100ns;
a1<='1';
b1<='0';


wait for 100ns;
a1<='1';
b1<='1';

wait;
end process;
end Behavioral;

```

## TBW Waveform

---

 

## XNOR Gate Dataflow Model

---

## VHD Code:

entity XNOR\_DF is

Port ( a : in STD\_LOGIC;

b : in STD\_LOGIC;

c : out STD\_LOGIC);

end XNOR\_DF;


architecture Dataflow of XNOR\_DF is

begin

c<=a XNOR b;

end Dataflow;

## RTL Diagram

 

## TBW Code:

```


entity XNOR_DF_TBW is
-- Port ( );
end XNOR_DF_TBW;
architecture Dataflow of XNOR_DF_TBW is
component XNOR_DF is
    Port ( a : in STD_LOGIC;
           b : in STD_LOGIC;
           c : out STD_LOGIC);
end component;
Signal a1:STD_LOGIC:='0';
Signal b1:STD_LOGIC:='0';
Signal c1:STD_LOGIC;
begin
UUT: XNOR_DF Port map(a=>a1, b=>b1, c=>c1);
stim_proc: process
begin
wait for 100ns;
a1<='0';
b1<='0';
wait for 100ns;
a1<='0';
b1<='1';
wait for 100ns;

a1<='1';
b1<='0';

```

```
wait for 100ns;  
a1<='1';  
b1<='1';  
wait;  
end process;  
end Dataflow;
```

## TBW Waveform

 

## XNOR Gate Behavioral Model



## **VHD Code:**


---

```
entity XNOR_GATE_BV is
    Port ( A : in STD_LOGIC;
          B : in STD_LOGIC;
          C : out STD_LOGIC);
end XNOR_GATE_BV;

architecture Behavioral of XNOR_GATE_BV is
begin
    process(A,B)
    begin
        if(A=B) then
            C<='1';
        else
            C<='0';
        end if;
    end process;
end Behavioral;
```

## **RTL Diagram**

---

 

## **TBW Code:**

---

entity XNOR\_GATE\_TBW is

-- Port ( );

end XNOR\_GATE\_TBW;

architecture Behavioral of XNOR\_GATE\_TBW is

component XNOR\_GATE\_BV is

Port ( A : in STD\_LOGIC;

B : in STD\_LOGIC;

C : out STD\_LOGIC);

end component;

Signal a1:STD\_LOGIC:='0';

Signal b1:STD\_LOGIC:='0';

Signal c1:STD\_LOGIC;

begin

UUT: XNOR\_GATE\_BV Port map(A=>a1, B=>b1, C=>c1);

stim\_proc: process

```

begin
wait for 100ns;
a1<='0';
b1<='0';

wait for 100ns;
a1<='0';
b1<='1';

wait for 100ns;
a1<='1';
b1<='0';


wait for 100ns;
a1<='1';
b1<='1';

wait;
end process;
end Behavioral;

```

## **TBW Waveform**

---

 

## **AND NAND Gate Dataflow Model**


---

## VHD Code:

```
entity AND_NAND_DF is
    Port ( A : in
           STD_LOGIC;
           B : in STD_LOGIC;
           C : out STD_LOGIC);
end AND_NAND_DF;

architecture Dataflow of AND_NAND_DF is
begin
    C<=(A NAND B) NAND (A NAND B);
end Dataflow;
```

## RTL Diagram

 

## TBW Code:

```
entity AND_NAND_TBW is
-- Port ( );
end AND_NAND_TBW;

architecture Dataflow of AND_NAND_TBW is
    component NAND_DF is
```

```

    Port ( A : in STD_LOGIC;
           B : in STD_LOGIC;
           C : out STD_LOGIC);
end component;

Signal a1:STD_LOGIC:='0';
Signal b1:STD_LOGIC:='0';
Signal c1:STD_LOGIC;

begin


UUT: AND_NAND_DF Port map(A=>a1, B=>b1, C=>c1);

stim_proc: process
begin
wait for 100ns;
a1<='0';
b1<='0';
wait for 100ns;
a1<='0';
b1<='1';
wait for 100ns;
a1<='1';
b1<='0';
wait for 100ns;
a1<='1';
b1<='1';
wait;
end process;

end Dataflow;

```

## TBW Waveform

 

## OR\_NAND Gate Dataflow Model

VHD Code:

entity OR\_NAND\_DF is

Port ( A : in STD\_LOGIC;

B : in STD\_LOGIC;

C : out STD\_LOGIC);

end OR\_NAND\_DF;

architecture Dataflow of OR\_NAND\_DF is


begin

C<=((A NAND A) NAND (B NAND B));

end Dataflow;

## RTL Diagram

---

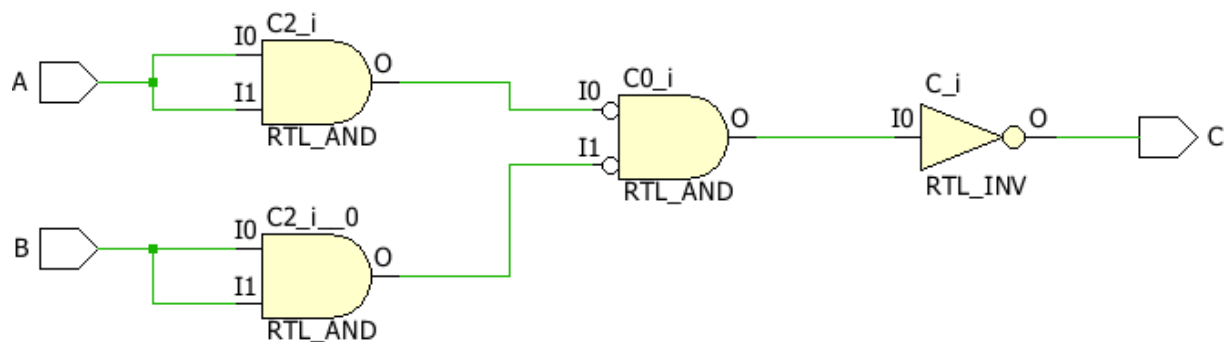

## TBW Code:

---

entity AND\_NAND\_TBW is

-- Port ( );

end AND\_NAND\_TBW;

architecture Dataflow of AND\_NAND\_TBW is

component NAND\_DF is

Port ( A : in

STD\_LOGIC;

B : in STD\_LOGIC;

C : out STD\_LOGIC);

end component;

Signal a1:STD\_LOGIC:='0';

Signal b1:STD\_LOGIC:='0';

Signal c1:STD\_LOGIC;

begin

UUT: AND\_NAND\_DF Port map(A=>a1, B=>b1, C=>c1);

stim\_proc: process

begin

wait for 100ns;

a1<='0';

b1<='0';

wait for 100ns;

a1<='0';

b1<='1';

wait for 100ns;

a1<='1';

b1<='0';

wait for 100ns;

a1<='1';

b1<='1';


wait;

end process;



```
end Dataflow;
```

## **TBW Waveform**

 

## **NOT NAND Gate Dataflow Model**

### **VHD Code:**

```
entity NOT_NAND_DF is
```

```
    Port ( A : in
```

```
          STD_LOGIC;
```

```
          B : out STD_LOGIC);
```

```

end NOT_NAND_DF;

architecture Dataflow of NOT_NAND_DF is
begin
B<=(A NAND A);
end Dataflow;

```

## RTL Diagram

---



## TBW Code:

---

```

entity NOT_NAND_TBW is
-- Port ( );
end NOT_NAND_TBW;

architecture Dataflow of NOT_NAND_TBW is
component NOT_NAND_DF is
    Port ( A : in STD_LOGIC;
          B : out STD_LOGIC);
end component;

Signal a1:STD_LOGIC:='0';
Signal b1:STD_LOGIC;
begin

```

```
UUT: NOT_NAND_DF Port map(A=>a1, B=>b1);
```

```
stim_proc: process
```

```
begin
```

```
wait for 100ns;
```

```
a1<='0';
```

```
wait for 100ns;
```

```
a1<='1';
```


```
wait;
```

```
end process;
```

```
end Dataflow;
```

## TBW Waveform

---

 

## XOR NAND Gate Dataflow Model

---

### VHD Code:

---

```
entity XOR_NAND_DF is
```

```
Port ( A : in
```

```
STD_LOGIC;
```

```
B : in STD_LOGIC;
```

```

        C : out STD_LOGIC);
end XOR_NAND_DF;

```


architecture Dataflow of XOR\_NAND\_DF is

```
begin
```

```
    C<=((A NAND A) NAND B) NAND (A NAND (B NAND B));
```

```
end Dataflow;
```

## RTL Diagram

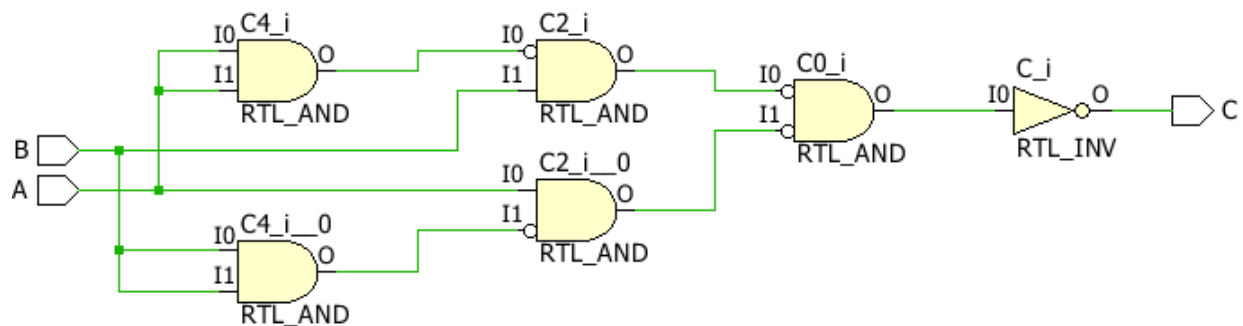

## TBW Code:

```
entity XOR_NAND_TBW is
```

```
-- Port ( );
```

```
end XOR_NAND_TBW;
```

architecture Dataflow of XOR\_NAND\_TBW is

```
component XOR_NAND_DF is
```

```
    Port ( A : in STD_LOGIC;
```

```

        B : in STD_LOGIC;
        C : out STD_LOGIC);
end component;
Signal a1:STD_LOGIC:='0';
Signal b1:STD_LOGIC:='0';
Signal c1:STD_LOGIC;
begin
UUT: XOR_NAND_DF Port map(A=>a1, B=>b1, C=>c1);
stim_proc: process
begin
wait for 100ns;
a1<='0';
b1<='0';
wait for 100ns;

a1<='0';
b1<='1';

wait for 100ns;

a1<='1';
b1<='0';


wait for 100ns;
a1<='1';
b1<='1';

```

```
wait;  
end process;  
end Dataflow;
```

## TBW Waveform

---

 

## XNOR NAND Gate Dataflow Model

---

### VHD Code:

---

```
entity XNOR_NAND_DF is  
    Port ( A : in STD_LOGIC;  
           B : in STD_LOGIC;
```

```

        C : out STD_LOGIC);
end XNOR_NAND_DF;

```

architecture Dataflow of XNOR\_NAND\_DF is

```
begin
```


```

C<=((A NAND A) NAND B) NAND (A NAND (B NAND B)) NAND ((A NAND A) NAND
B) NAND (A NAND (B NAND B));

```

```
end Dataflow;
```

## RTL Diagram

 

## TBW Code:

```
entity XNOR_NAND_TBW is
```

```
-- Port ( );
```

```
end XNOR_NAND_TBW;
```

architecture Dataflow of XNOR\_NAND\_TBW is

component XNOR\_NAND\_DF is

```
Port ( A : in
```

```
STD_LOGIC; B : in
```

```
STD_LOGIC;
```

```

        C : out STD_LOGIC);

end component;

Signal a1:STD_LOGIC:='0';
Signal b1:STD_LOGIC:='0';
Signal c1:STD_LOGIC;

begin

UUT: XNOR_NAND_DF Port map(A=>a1, B=>b1, C=>c1);

stim_proc: process
begin

wait for 100ns;

a1<='0';
b1<='0';

wait for 100ns;


a1<='0';
b1<='1';


wait for 100ns;


a1<='1';
b1<='0';


wait for 100ns;

a1<='1';
b1<='1';

wai

```



# AND NOR Gate Dataflow Model

## VHD Code:


```
entity AND_NOR_DF is
    Port ( A : in STD_LOGIC;
           B : in STD_LOGIC;
           C : out STD_LOGIC);
end AND_NOR_DF;
architecture Dataflow of AND_NOR_DF is

begin

    C<=((A NOR A) NOR (B NOR B));

end Dataflow;
```

## RTL Diagram

 

## TBW Code:

```
entity AND_NOR_TBW is
    -- Port ( );
end AND_NOR_TBW;

architecture Dataflow of AND_NOR_TBW is

    component AND_NOR_DF is
        Port ( A : in STD_LOGIC;
               B : in STD_LOGIC;
```

```

        C : out STD_LOGIC);

end component;

Signal a1:STD_LOGIC:='0'
Signal b1:STD_LOGIC:='0';

Signal c1:STD_LOGIC;

begin

UUT: AND_NOR_DF Port map(A=>a1, B=>b1, C=>c1);

stim_proc: process

begin

wait for 100ns;

a1<='0';
b1<='0';

wait for 100ns;


a1<='0';
b1<='1';


wait for 100ns;


a1<='1';
b1<='0';


wait for 100ns;

a1<='1';
b1<='1';


wait;

end process;

end Dataflow;

```

## TBW Waveform

 

## OR NOR Gate Dataflow Model

### VHD Code:

entity OR\_NOR\_GATE\_DF is

Port ( A : in STD\_LOGIC;

B : in STD\_LOGIC;

C : out STD\_LOGIC);

end OR\_NOR\_GATE\_DF;

architecture Dataflow of OR\_NOR\_GATE\_DF is

```


begin

C<=(A NOR B) NOR (A NOR B);

end Dataflow;

```

## **RTL Diagram**

 

## **TBW Code:**

```

entity OR_NOR_TBW is
-- Port ( );
end OR_NOR_TBW;

architecture Dataflow of OR_NOR_TBW is
component OR_NOR_GATE_DF is
    Port ( A : in STD_LOGIC;
           B : in STD_LOGIC;
           C : out STD_LOGIC);
end component;

Signal a1:STD_LOGIC:='0';
Signal b1:STD_LOGIC:='0';
Signal c1:STD_LOGIC;

begin

UUT: OR_NOR_GATE_DF Port map(A=>a1, B=>b1, C=>c1);

stim_proc: process
begin
wait for 100ns;

a1<='0';

b1<='0';

```

```
wait for 100ns;
```

```
a1<='0';
```

```
b1<='1';
```

```
wait for 100ns;
```

```
a1<='1';
```

```
b1<='0';
```

```
wait for 100ns;
```

```
a1<='1';
```


```
b1<='1';
```

```
wait;
```

```
end process;
```

```
end Dataflow;
```

## TBW Waveform

 

## NOT NOR Gate Dataflow Model

### VHD Code:

```
entity NOT_NOR _DF is
```


```

Port ( A : in STD_LOGIC;
      B : out STD_LOGIC);
end NOT_NOR_DF;

architecture Dataflow of NOT_NOR_DF is
begin
B<=(A NOR A);
end Dataflow;

```

## RTL Diagram

 

## TBW Code:

```

entity NOT_NOR_TBW is
-- Port ( );
end NOT_NOR_TBW;

architecture Dataflow of NOT_NOR_TBW is
component NOT_NOR_DF is
Port ( A : in STD_LOGIC;
      B : out STD_LOGIC);
end component;

Signal a1:STD_LOGIC:='0';
Signal b1:STD_LOGIC;

begin

UUT: NOT_NOR_DF Port map(A=>a1, B=>b1);

stim_proc: process
begin
wait for 100ns;

```

```

a1<='0';

wait for 100ns;
a1<='1';


wait;

end process;

end Dataflow;

```

## **TBW Waveform**

 

## **XOR NOR Gate Dataflow Model**

### **VHD Code:**

```

entity XOR_NOR_GATE_DF is
    Port ( A : in STD_LOGIC;
           B : in STD_LOGIC;
           C : out STD_LOGIC);
end XOR_NOR_GATE _DF;

architecture Dataflow of XOR_NOR _GATE_DF is


begin

```

```
C<=((A NOR A) NOR B) NOR (A NOR (B NOR B)) NOR ((A NOR A) NOR B) NOR (A NOR
(B NOR B));
```

```
end Dataflow;
```

## RTL Diagram

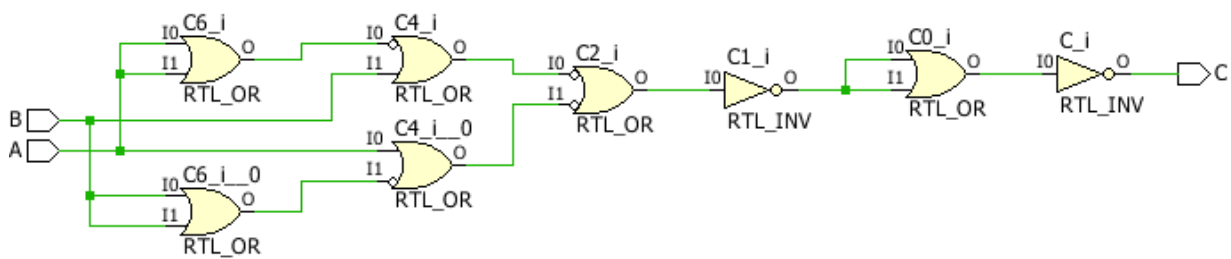

## TBW Code:

```
entity XOR_NOR_TBW is
```

```
-- Port ( );
```

```
end XOR_NOR_TBW;
```

```
architecture Dataflow of XOR_NOR_TBW is
```

```
component XOR_NOR_GATE_DF is
```

```
Port ( A : in STD_LOGIC;
```

```
      B : in STD_LOGIC;
```

```
      C : out STD_LOGIC);
```

```
end component;
```

```
Signal a1:STD_LOGIC:='0';
```

```
Signal b1:STD_LOGIC:='0';
```



```
Signal c1:STD_LOGIC;

begin

UUT: XOR_NOR_GATE _DF Port map(A=>a1, B=>b1, C=>c1);

stim_proc: process

begin

wait for 100ns;

a1<='0';

b1<='0';

wait for 100ns;


a1<='0';

b1<='1';


wait for 100ns;


a1<='1';

b1<='0';


wait for 100ns;

a1<='1';


b1<='1';

wait;

end process;

end Dataflow;
```

## **TBW Waveform**

 

## XNOR NOR Gate Dataflow Model

### VHD Code:

entity XNOR\_NOR\_DF is

Port ( A : in STD\_LOGIC;

B : in STD\_LOGIC;

C : out STD\_LOGIC);

end XNOR\_NOR\_DF;


architecture Dataflow of XNOR\_NOR\_DF is

begin

C<=((A NOR A) NOR B) NOR (A NOR (B NOR B));

end Dataflow;

### RTL Diagram

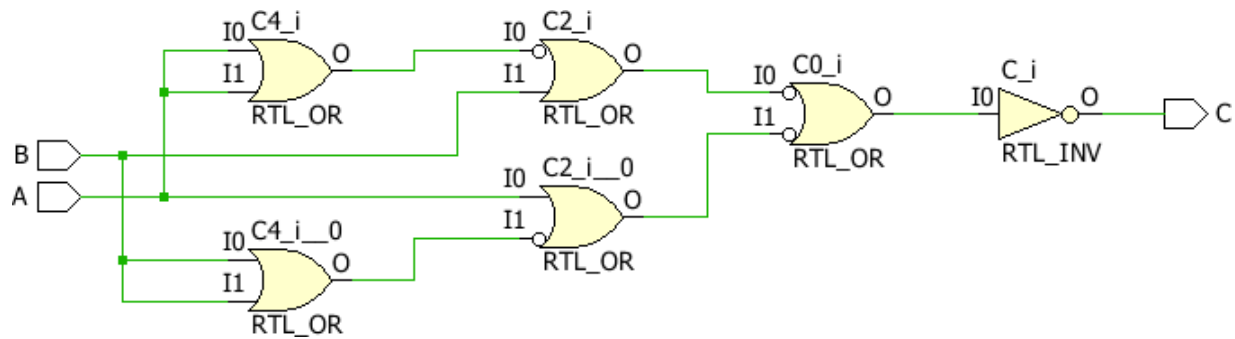

## **TBW Code:**

entity XNOR\_NOR\_TBW is

-- Port ( );

end XNOR\_NOR\_TBW;

architecture Dataflow of XNOR\_NOR\_TBW is

component XNOR\_NOR\_DF is

Port ( A : in STD\_LOGIC;

B : in STD\_LOGIC;

C : out STD\_LOGIC);

end component;

Signal a1:STD\_LOGIC:='0';

Signal b1:STD\_LOGIC:='0';

Signal c1:STD\_LOGIC;

begin

```
UUT: XNOR_NOR_DF Port map(A=>a1, B=>b1, C=>c1);
```

```
stim_proc: process
```

```
begin
```

```
wait for 100ns;
```

```
a1<='0';
```

```
b1<='0';
```

```
wait for 100ns;
```

```
a1<='0';
```

```
b1<='1';
```

```
wait for 100ns;
```

```
a1<='1';
```

```
b1<='0';
```

```
wait for 100ns;
```

```
a1<='1';
```


```
b1<='1';
```

```
wait;
```

```
end process;
```

```
end Dataflow;
```

## TBW Waveform

 

# HALF ADDER Dataflow Model


## VHD Code:

```
entity HALF_ADDER_DF is
    Port ( A : in STD_LOGIC;
          B : in STD_LOGIC;
          S : out STD_LOGIC;
          C : out STD_LOGIC);
end HALF_ADDER_DF;

architecture Dataflow of HALF_ADDER_DF is
begin
    S<=A xor B;
    C<=A and B;

end Dataflow
```

## RTL Diagram

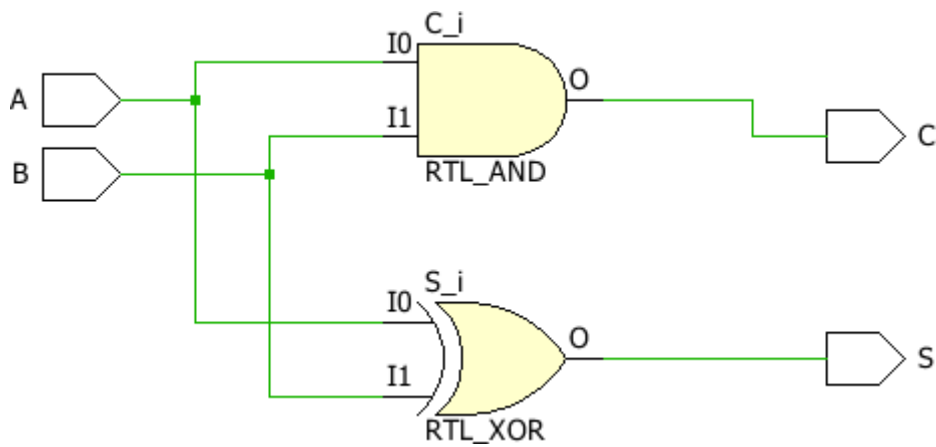

## TBW Code:

entity HALF\_ADDER\_TBW is

-- Port ( );

end HALF\_ADDER\_TBW;

architecture Behavioral of HALF\_ADDER\_TBW is

component HALF\_ADDER\_BV is

Port ( A : in

STD\_LOGIC; B: in

STD\_LOGIC; S: out

STD\_LOGIC;

C : out STD\_LOGIC);

end component;

Signal a1:STD\_LOGIC:='0';

Signal b1:STD\_LOGIC:='0';


```
Signal s1:STD_LOGIC;
Signal c1:STD_LOGIC;

begin

UUT: HALF_ADDER_BV Port map(A=>a1, B=>b1, S=>s1, C=>c1);

stim_proc: process
begin
wait for 100ns;
a1<='0';
b1<='0';
wait for 100ns;
a1<='0';
b1<='1';
wait for 100ns;
a1<='1';
b1<='0';
wait for 100ns;
a1<='1';
b1<='1';
wait;
end process;
end Behavioral;
```

## **TBW Waveform**

 

## HALF ADDER Behavioral Model

### VHD Code:

```

entity HALF_ADDER_BV is
Port ( A : in STD_LOGIC;
      B : in STD_LOGIC;
      S : out STD_LOGIC;
      C : out STD_LOGIC);
end HALF_ADDER_BV;

architecture Behavioral of HALF_ADDER_BV is
begin
process(A,B)
begin
    if(A=B) then

```




```

        S<='0';
    else
        S<='1';
    end if;

    if(A='1' and B='1') then
        C<='1';
    else
        C<='0';
    end if;
end process; end Behavioral;

```

## RTL Diagram:

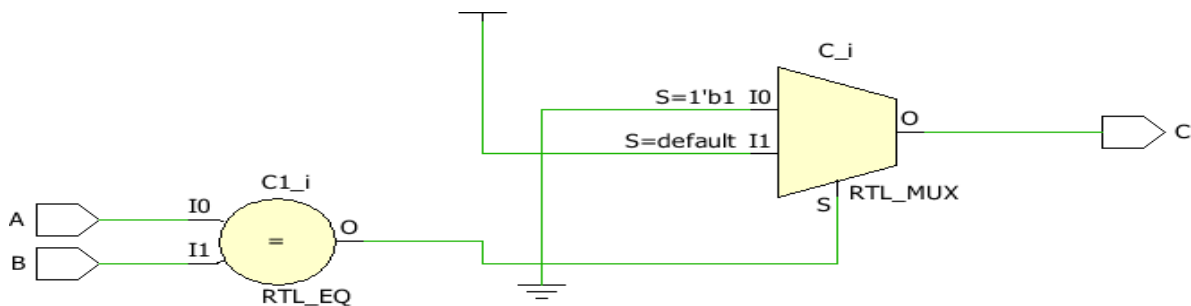

## TBW Code:

```

entity HALF_ADDER_TBW is
-- Port ( );
end HALF_ADDER_TBW;

architecture Behavioral of HALF_ADDER_TBW is
component HALF_ADDER_BV is
    Port ( A : in STD_LOGIC;

```

```

        B: in STD_LOGIC;

        S: out STD_LOGIC;

        C : out STD_LOGIC);

end component;

Signal a1:STD_LOGIC:='0';

Signal

b1:STD_LOGIC:='0';

Signal s1:STD_LOGIC;

Signal c1:STD_LOGIC;

begin

UUT: HALF_ADDER_BV Port map(A=>a1, B=>b1, S=>s1, C=>c1);

stim_proc: process

begin

wait for 100ns;

a1<='0';

b1<='0';

wait for 100ns;

a1<='0';

b1<='1';

wait for 100ns;

a1<='1';

b1<='0';

wait for 100ns;

a1<='1';

b1<='1';


wait;

end process;

```

end Behavioral;

## **TBW Waveform:**

 

## **HALF ADDER Structural Model**

### **VHD Code:**

Entity HALF\_ADDER\_structural is

Port ( x : in STD\_LOGIC;

      y : in STD\_LOGIC;

      sum : out STD\_LOGIC;

      carry : out STD\_LOGIC);

end HALF\_ADDER\_structural;

architecture Structural of HALF\_ADDER\_structural is

component XOR\_DF is

Port ( A : in STD\_LOGIC;

      B : in STD\_LOGIC;

      C : out STD\_LOGIC);

end component;

component AND\_DF is

Port ( A : in STD\_LOGIC;

B : in STD\_LOGIC;

C : out STD\_LOGIC);

end component;


begin

I1:XOR\_DF port map(x,y,sum);

I2:AND\_DF port map(x,y,carry);

end Structural;

## **RTL Diagram**

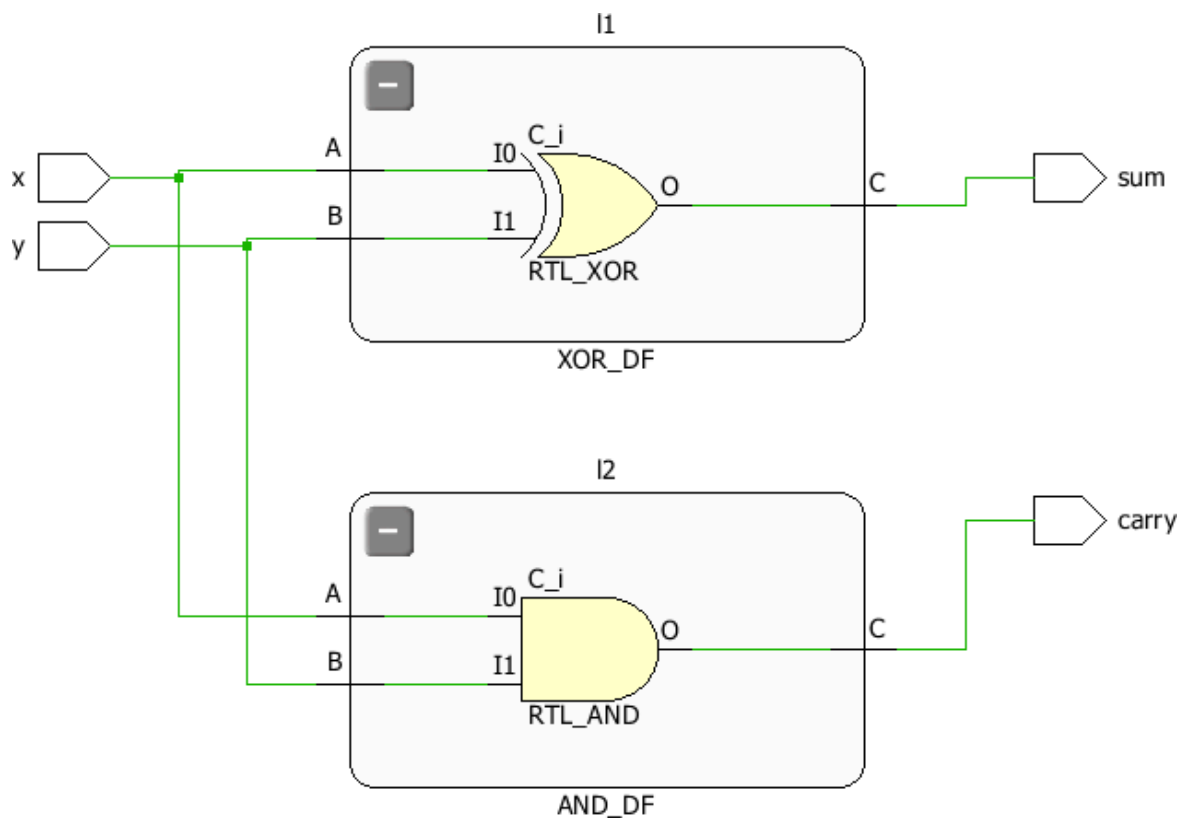

## **TBW Code:**

entity HALF\_ADDER\_structural is

```
Port ( x : in STD_LOGIC;  
      y : in STD_LOGIC;  
      sum : out STD_LOGIC;  
      carry : out STD_LOGIC);
```

end HALF\_ADDER\_structural;

architecture Structural of HALF\_ADDER\_structural is

component XOR\_DF is

```
Port ( A : in STD_LOGIC;  
      B : in STD_LOGIC;  
      C : out STD_LOGIC);
```

end component;

component AND\_DF is

```
Port ( A : in STD_LOGIC;  
      B : in STD_LOGIC;  
      C : out STD_LOGIC);
```

end component;


begin

I1:XOR\_DF port map(x,y,sum);

I2:AND\_DF port map(x,y,carry);

end Structural;

## **TBW Waveform**

 


## FULL ADDER Dataflow Model

### VHD Code:

```
entity FULL_ADDER_DF is
    Port ( A : in STD_LOGIC;
          B : in STD_LOGIC;
          Cin : in STD_LOGIC;
          S : out STD_LOGIC;
          Cout : out STD_LOGIC);
end FULL_ADDER_DF;

architecture Behavioral of FULL_ADDER_DF is
begin
    S<=(A xor B) xor Cin;
    Cout<=(A and B) or (B and Cin) or (Cin and A);
end Behavioral;
```

## RTL Diagram

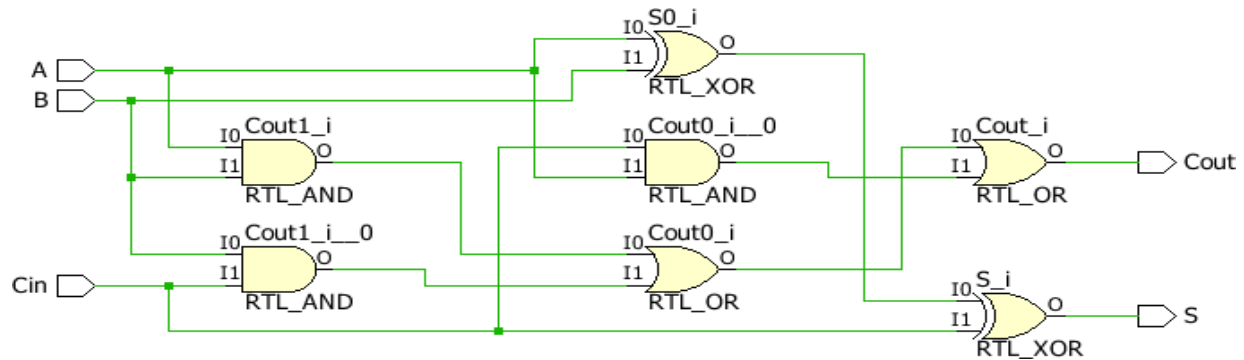

## TBW Code:

entity FULL\_ADDER\_TBW is

-- Port ( );

end FULL\_ADDER\_TBW;

architecture Behavioral of FULL\_ADDER\_TBW is

component FULL\_ADDER\_BV is

Port ( A : in

AI Page Translation is now live! [Click here](#)

to set it up.

STD\_LOGIC; B: in

STD\_LOGIC; S: out

STD\_LOGIC;

C : out STD\_LOGIC);

end component;

Signal a1:STD\_LOGIC:= '0';

Signal

b1:STD\_LOGIC:= '0';

Signal s1:STD\_LOGIC;

Signal c1:STD\_LOGIC;

begin

UUT: FULL\_ADDER\_BV Port map(A=>a1, B=>b1, S=>s1, C=>c1);

```

stim_proc: process
begin
wait for 100ns;
a1<='0';
b1<='0';

wait for 100ns;
a1<='0';
b1<='1';


wait for 100ns;
a1<='1';
b1<='0';

wait for 100ns;
a1<='1';
b1<='1';

wait;
end process;
end Behavioral;

```

## TBW Waveform

 



## FULL ADDER Behavioral Model

### VHD Code:

```
entity FULL_ADDER_BV is
  Port ( A : in STD_LOGIC;
        B : in STD_LOGIC;
        Cin: in STD_LOGIC;
        S : out STD_LOGIC;
        Cout : out STD_LOGIC);
end FULL_ADDER_BV;
```

architecture Behavioral of FULL\_ADDER\_BV is

begin

process(A,B,Cin)

begin

if((A='0') and (B=Cin)) then

S<='0';

else

S<='1';

end if;

if((A='1') and (B=Cin)) then

S<='1';

else

S<='0';

end if;

if((A='0') and (B='1' and Cin='1')) then

Cout<='1';

else

Cout<='0';

end if;

if((A='1') and (B='0' and Cin='0')) then

Cout<='0';

else


Cout<='1';

end if;

end process;

end Behavioral;

## RTL Diagram

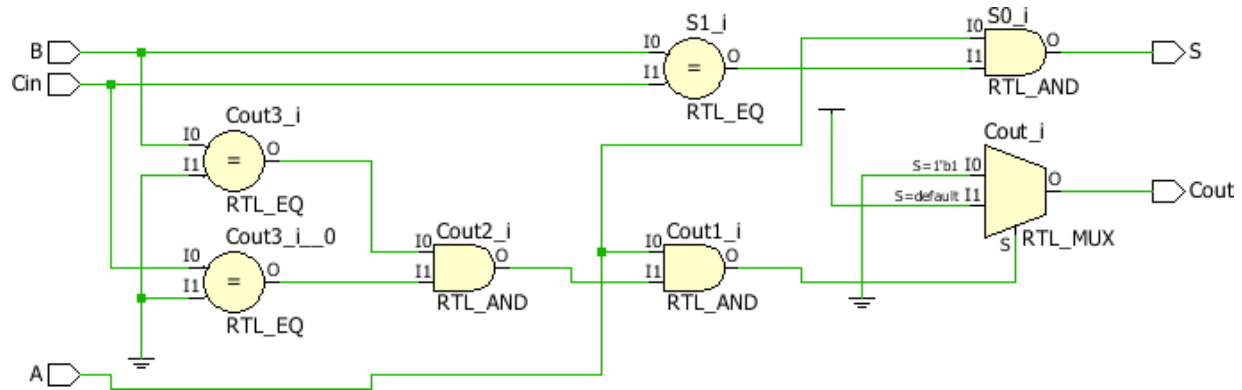

## TBW Code:

entity FULL\_ADDER\_TBW is

-- Port ( );

end FULL\_ADDER\_TBW;

architecture Behavioral of FULL\_ADDER\_TBW is

component FULL\_ADDER\_BV is

Port ( A : in

STD\_LOGIC; B: in

STD\_LOGIC; S: out

STD\_LOGIC;

C : out STD\_LOGIC);


end component;

Signal a1:STD\_LOGIC:='0';

```
Signal b1:STD_LOGIC:='0';
Signal s1:STD_LOGIC;
Signal c1:STD_LOGIC;
begin
UUT: FULL_ADDER_BV Port map(A=>a1, B=>b1, S=>s1, C=>c1);

stim_proc: process
begin
wait for 100ns;
a1<='0';
b1<='0';
wait for 100ns;
a1<='0';
b1<='1';
wait for 100ns;
a1<='1';
b1<='0';
wait for 100ns;
a1<='1';
b1<='1';
wait;
end process;
end Behavioral;
```

## **TBW Waveform**

 

## FULL ADDER Structural Model

### VHD Code:

entity FULL\_ADDER\_structural is

Port ( x : in STD\_LOGIC;

y : in STD\_LOGIC;

z : in STD\_LOGIC;

sum : out STD\_LOGIC;

carry : out STD\_LOGIC);

end FULL\_ADDER\_structural;

architecture Structural of FULL\_ADDER\_structural is

component HALF\_ADDER\_DF is

Port ( A : in STD\_LOGIC;

B : in STD\_LOGIC;

S : out STD\_LOGIC;

C : out STD\_LOGIC);

end component;

component OR\_DF is

Port ( a : in STD\_LOGIC;

b : in STD\_LOGIC;

c : out STD\_LOGIC);

end component;

signal s1:std\_logic;

signal c1:std\_logic;

signal c2:std\_logic;

begin


I1:HALF\_ADDER\_DF port map(x,y,s1,c1);

I2:HALF\_ADDER\_DF port map(s1,z,sum,c2);

I3:OR\_DF port map(c1,c2,carry);

end Structural;

## **RTL Diagram**

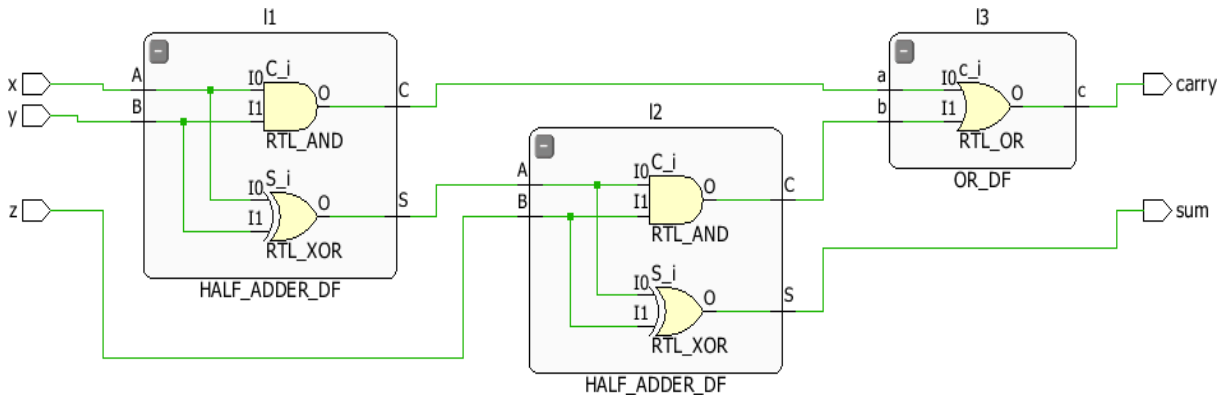

## **TBW Code:**

entity FULL\_ADDER\_TBW is

-- Port ( );

end FULL\_ADDER\_TBW;

architecture Structural of FULL\_ADDER\_TBW is

component FULL\_ADDER\_structural is

Port ( x : in STD\_LOGIC;

y: in STD\_LOGIC;

z: in STD\_LOGIC;

sum: out STD\_LOGIC;

carry : out STD\_LOGIC);

end component;

Signal x1:STD\_LOGIC:='0';

Signal y1:STD\_LOGIC:='0';

Signal z1:STD\_LOGIC:='0';

Signal s1:STD\_LOGIC;

Signal c1:STD\_LOGIC;

begin

```
UUT: FULL_ADDER_structural Port map(x=>x1, y=>y1, z=>z1, sum=>s1,  
carry=>c1);
```

```
stim_proc: process
```

```
begin
```

```
wait for 50ns;
```

```
x1<='0';
```

```
y1<='0';
```

```
z1<='1';
```

```
wait for 50ns;
```

```
x1<='0';
```

```
y1<='1';
```

```
z1<='0';
```

```
wait for 50ns;
```

```
x1<='0';
```

```
y1<='1';
```

```
z1<='1';
```

```
wait for 50ns;
```

```
x1<='1';
```

```
y1<='0';
```

```
z1<='0';
```

```
wait for 50ns;
```

```
x1<='1';
```

```
y1<='0';
```

```
z1<='1';
```

```
wait for 50ns;
```

```
x1<='1';
```

```
y1<='1';
```

```
z1<='0';
```

```
wait for 50ns;
```



```

x1<='1';
y1<='1';

z1<='1';


wait for 50ns;

end process;

end Structural;

```

## TBW WaveForm

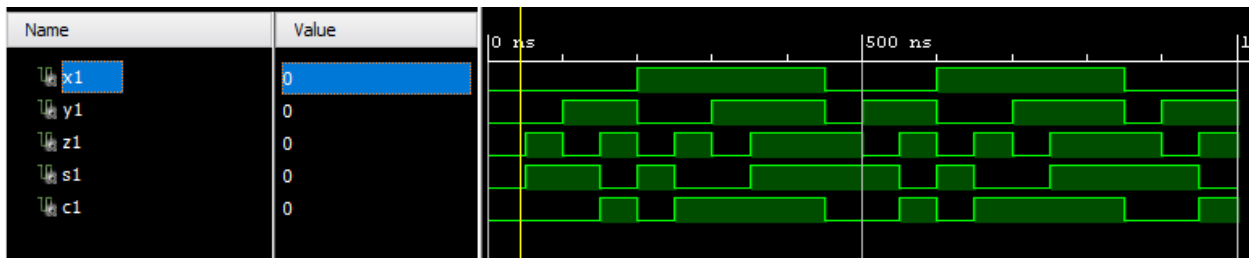

## 2:1 MUX Dataflow Model

---

### VHD Code:

---

```


entity MUX_2_1_DF is
  Port ( I0 : in STD_LOGIC;
        I1 : in STD_LOGIC;
        S : in STD_LOGIC;
        Y : out STD_LOGIC);
end MUX_2_1_DF;
architecture Dataflow of MUX_2_1_DF is
begin
  Y<=((NOT S) AND I0) OR (S AND I1);
end Dataflow;

```

---

## RTL Diagram

---

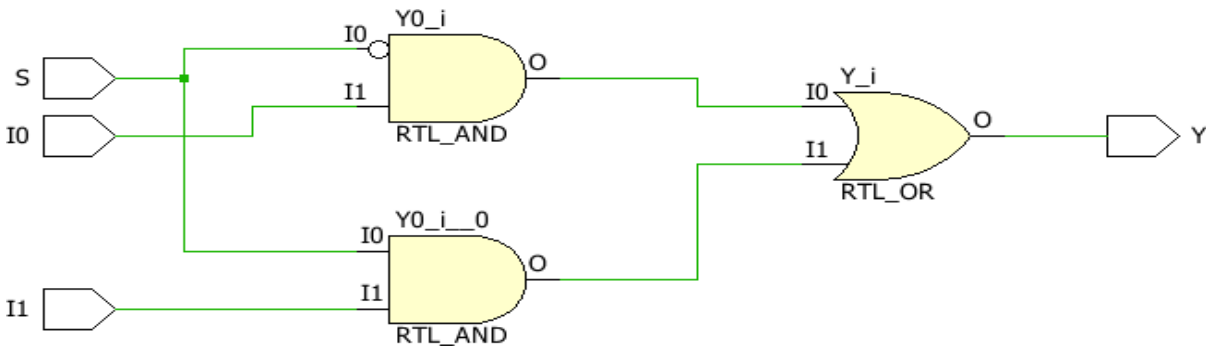

## TBW Code:

---

entity MUX\_2\_1\_TBW is

-- Port ( );

end MUX\_2\_1\_TBW;

architecture Dataflow of MUX\_2\_1\_TBW is

component MUX\_2\_1\_BV is

Port ( I0 : in STD\_LOGIC;

I1 : in STD\_LOGIC;

S : in STD\_LOGIC;

Y : out STD\_LOGIC);

end component;

signal i01: STD\_LOGIC:='0';

signal i11: STD\_LOGIC:='0';

signal s1: STD\_LOGIC:='0';

signal y1: STD\_LOGIC;

begin

UUT: MUX\_2\_1\_DF Port map(I0=>i01, I1=>i11, S=>s1, Y=>y1);


```

stim_proc: process
begin
wait for 100ns;
s1<='0';
wait for 100ns;
s1<='1';
wait;
end process;
end Dataflow;

```

## TBW Waveform

---

 

## 2:1 MUX Behavioral Model

---

### VHD Code:

---

```

entity MUX_2_1_DF is
  Port ( I0 : in STD_LOGIC;
        I1 : in STD_LOGIC;
        S : in STD_LOGIC;
        Y : out STD_LOGIC);
end MUX_2_1_DF;
architecture Behavioral of MUX_2_1_DF is
begin
  process(I0,I1,S)
  begin
    if(S='0') then
      Y <= I0;
    else
      Y<= I1;
    end if;
  end process;
end Behavioral;


```

---

---

## RTL Diagram

---

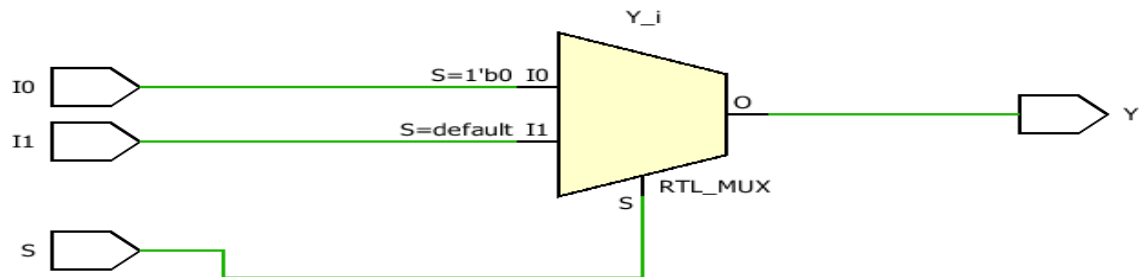

## TBW Code:

---

entity MUX\_2\_1\_TBW is

-- Port ( );

end MUX\_2\_1\_TBW;

architecture Behavioral of MUX\_2\_1\_TBW is

component MUX\_2\_1\_DF is

```
Port ( I0 : in STD_LOGIC;  
      I1: in STD_LOGIC;  
      S: in STD_LOGIC;  
      Y : out STD_LOGIC);
```

end component;

Signal i01:STD\_LOGIC:='0';

Signal i11:STD\_LOGIC:='0';

Signal s1:STD\_LOGIC:='0';

Signal y1:STD\_LOGIC;

begin

UUT: MUX\_2\_1\_DF Port map(I0=>i01, I1=>i11, S=>s1, Y=>y1);

stim\_proc: process

begin

wait for 100ns;

s1<='1';


wait;

end process;

end Behavioral;

## TBW Waveform

---

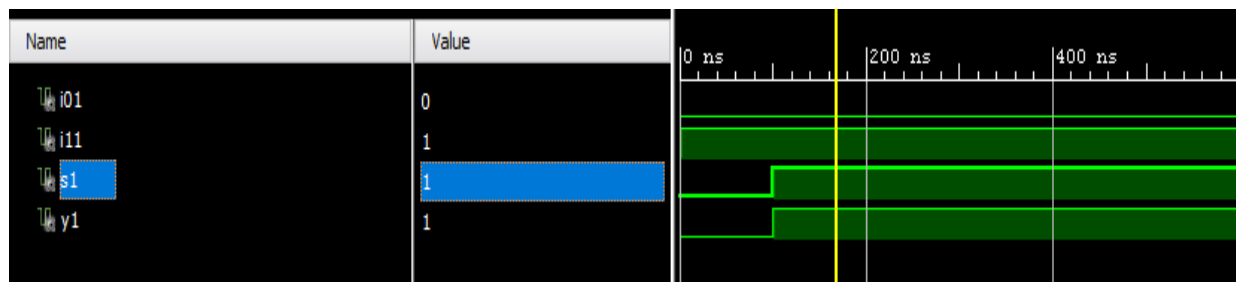

## 2:1 MUX Dataflow Model

---

### VHD Code:


---

```
entity MUX_2_1_dataflow is
    Port ( I0 : in STD_LOGIC;
          I1 : in STD_LOGIC;
          S  : in STD_LOGIC;
          Y  : out STD_LOGIC);
end MUX_2_1_dataflow;

architecture Dataflow of MUX_2_1_dataflow is
begin
    Y <= (((not S) and I0) or (S and I1));
end Dataflow;
```

### RTL Diagram

---

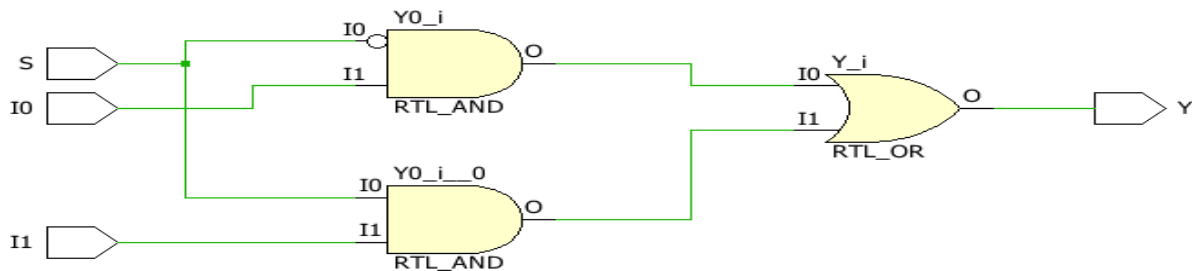

### TBW Code:

---

```
entity MUX_2_1_TBW is
-- Port ( );
```

```

end MUX_2_1_TBW;

architecture Behavioral of MUX_2_1_TBW is
component MUX_2_1_DF is
    Port ( I0 : in STD_LOGIC;
           I1: in STD_LOGIC;
           S: in STD_LOGIC;
           Y : out STD_LOGIC);
end component;

Signal i01:STD_LOGIC:='0';
Signal i11:STD_LOGIC:='0';
Signal s1:STD_LOGIC:='0';
Signal y1:STD_LOGIC;

begin


UUT: MUX_2_1_DF Port map(I0=>i01, I1=>i11, S=>s1, Y=>y1);

stim_proc: process
begin
wait for 100ns;
s1<='1';
wait;
end process;
end Behavioral;

```

## TBW Waveform

---

 

## 4:1 MUX Dataflow Model

---

### VHD Code:

---

```
entity MUX_4_1_DF is
  Port ( IP : in STD_LOGIC_VECTOR (3 downto 0);
        S : in STD_LOGIC_VECTOR (1 downto 0);
        Y : out STD_LOGIC);
end MUX_4_1_DF;
architecture Dataflow of MUX_4_1_DF is
begin
  Y <= IP(0) when S="00" else
    IP(1) when S="01" else
    IP(2) when S="10" else
    IP(3);


end Dataflow;
```

---

### RTL Diagram

---



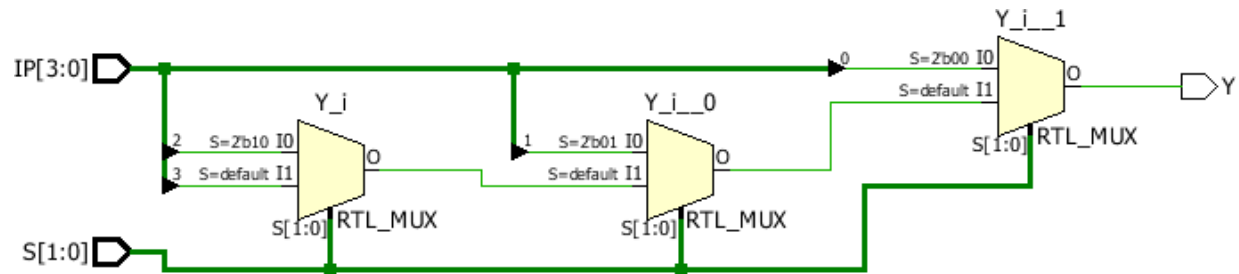

## TBW Code:

```
entity MUX_4_1_TBW is
-- Port ( );
end MUX_4_1_TBW;

architecture Behavioral of MUX_4_1_TBW is
component MUX_4_1_BV is
    Port ( IP : in STD_LOGIC_VECTOR (3 downto 0);
          S : in STD_LOGIC_VECTOR (1 downto 0);
          Y : out STD_LOGIC);
end component;

begin
    UUT: MUX_4_1_BV Port map(IP=>IP, S=>S, Y=>y1);


    stim_proc: process
    begin
```

```

wait for 100ns;
S(0)<='0';
S(1)<='1';
wait for 100ns;
S(0)<='1';
S(1)<='0';
wait for 100ns;
S(0)<='1';
S(1)<='1';
wait;
end process;
end Behavioral;

```

## TBW Waveform

 

## 4:1 MUX Behavioral Model

---

### **VHD Code:**

---

```
entity MUX_4_1_BV is
    Port ( IP : in STD_LOGIC_VECTOR (3 downto 0);
          S  : in STD_LOGIC_VECTOR (1 downto 0);
          Y  : out STD_LOGIC);
end MUX_4_1_BV;

architecture Behavioral of MUX_4_1_BV is
begin
    process(IP,S)
    begin
        case S is
            when "00" => Y <= IP(0);
            when "01" => Y <= IP(1);
            when "10" => Y <= IP(2);
            when "11" => Y <= IP(3);
```

```

        when others => NULL;


    end case;

end process;

end Behavioral;

```

## RTL Diagram

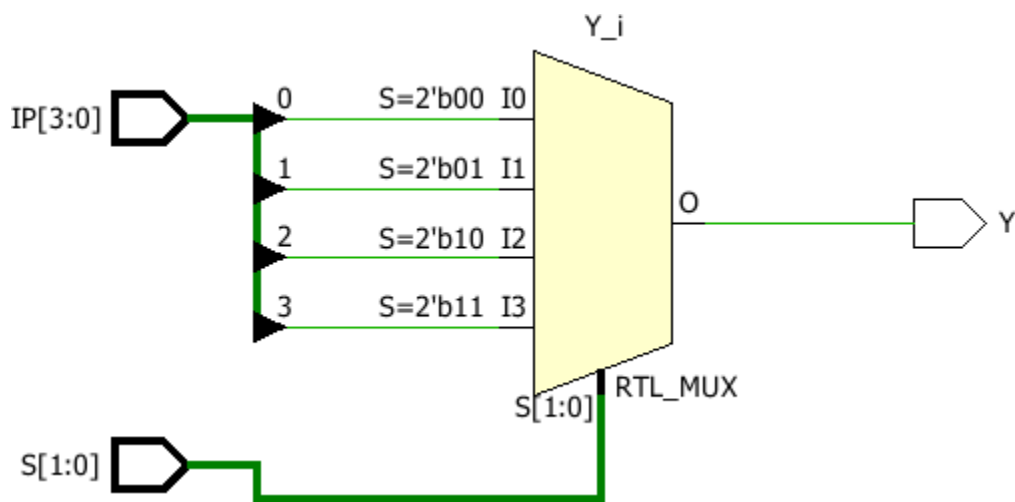

## TBW Code:

```

entity MUX_4_1_TBW is
-- Port ( );
end MUX_4_1_TBW;

architecture Behavioral of MUX_4_1_TBW is
component MUX_4_1_BV is
    Port ( IP : in STD_LOGIC_VECTOR (3 downto 0);
          S : in STD_LOGIC_VECTOR (1 downto 0);

```


```

        Y : out STD_LOGIC);
end component;
Signal IP:STD_LOGIC_VECTOR(3 downto 0):="1010";
Signal S:STD_LOGIC_VECTOR(1 downto 0):="00";
Signal y1:STD_LOGIC;
begin
UUT: MUX_4_1_BV Port map(IP=>IP, S=>S, Y=>y1);
stim_proc: process
begin
wait for 100ns;
S(0)<='0';
S(1)<='1';
wait for 100ns;
S(0)<='1';
S(1)<='0';
wait for 100ns;
S(0)<='1';
S(1)<='1';
wait;
end process;
end Behavioral;

```

## **TBW Waveform**

---

 

## 3:8 Decoder Dataflow Model

### VHD Code:

---

entity DECODER\_3\_8\_DF is

Port ( IP : in STD\_LOGIC\_VECTOR (2 downto 0);

OP : out STD\_LOGIC\_VECTOR (7 downto 0));

end DECODER\_3\_8\_DF;

architecture Dataflow of DECODER\_3\_8\_DF is

begin

OP(0) <='1' when IP = "000" else '0';

OP(1) <='1' when IP = "001" else '0';

OP(2) <='1' when IP = "010" else '0';

OP(3) <='1' when IP = "011" else '0';

OP(4) <='1' when IP = "100" else '0';

```

OP(5) <='1' when IP = "101" else '0';
OP(6) <='1' when IP = "110" else '0';
OP(7) <='1' when IP = "111" else '0';

```


```

end Dataflow;

```

## RTL Diagram

---

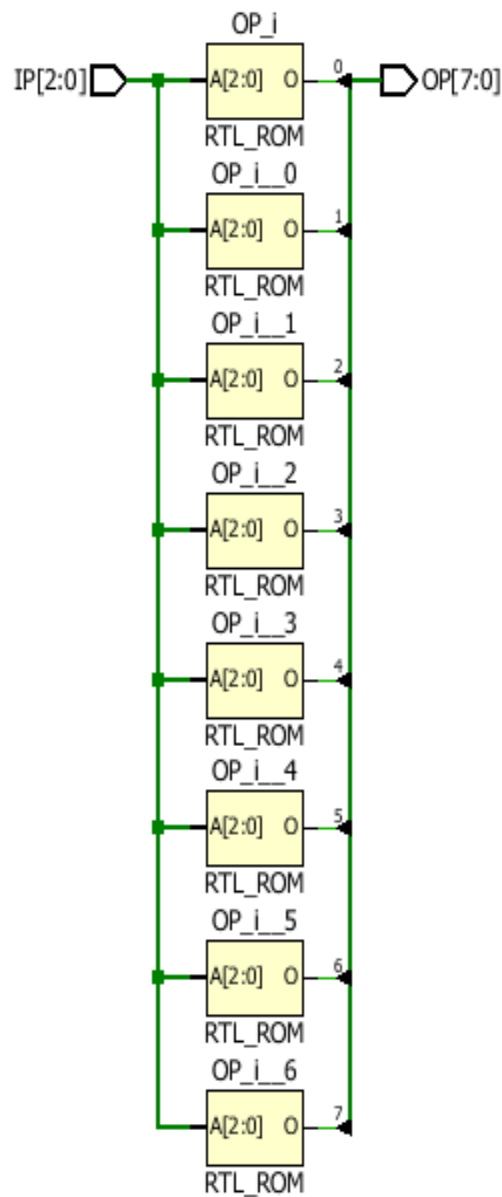

## TBW Code:

---

```
entity DECODER_3_8_TBW is
-- Port ( );
end DECODER_3_8_TBW;
architecture Dataflow of DECODER_3_8_TBW is
component DECODER_3_8_DF is
    Port ( IP : in STD_LOGIC_VECTOR (2 downto 0);
          OP : out STD_LOGIC_VECTOR (7 downto 0));
end component;
Signal IP:STD_LOGIC_VECTOR(2 downto 0):="000";
Signal OP:STD_LOGIC_VECTOR(7 downto 0);
begin
UUT: DECODER_3_8_DF Port map(IP=>IP, OP=>OP);
stim_proc: process
begin
wait for 100ns;
IP(0)<='0';
IP(1)<='0';
IP(2)<='1';
wait for 100ns;
IP(0)<='0';
IP(1)<='1';
IP(2)<='0';
wait for 100ns;
IP(0)<='0';
IP(1)<='1';
IP(2)<='1';
wait for 100ns;
IP(0)<='1';
```




```

IP(1)<='0';
IP(2)<='0';
wait for 100ns;
IP(0)<='1';
IP(1)<='0';
IP(2)<='1';
wait for 100ns;
IP(0)<='1';
IP(1)<='1';
IP(2)<='0';
wait for 100ns;
IP(0)<='1';
IP(1)<='1';
IP(2)<='1';
wait;
end process;
end Dataflow;

```

## TBW Waveform

 

## 3:8 Decoder Behavioral Model

### VHD Code:

entity Decoder\_3\_8\_BV is

```

Port ( IP : in STD_LOGIC_VECTOR (2 downto 0);
      OP : out STD_LOGIC_VECTOR (7 downto 0));

end Decoder_3_8_BV;

```

architecture Behavioral of Decoder\_3\_8\_BV is

```
begin process(IP)
```

```
begin
```

```
  OP<="00000000";
```

```
  case IP is
```

```
    when "000" => OP(0) <= '1';
```

```
    when "001" => OP(1) <= '1';
```

```
    when "010" => OP(2) <= '1';
```

```
    when "011" => OP(3) <= '1';
```

```
    when "100" => OP(4) <= '1';
```

```
    when "101" => OP(5) <= '1';
```

```
    when "110" => OP(6) <= '1';
```

```
    when "111" => OP(7) <= '1';
```


```
    when others => NULL;
```

```
  end case;
```

```
end process;
```

```
end Behavioral;
```

## RTL Diagram

 

## **TBW Code:**

entity DECODER\_3\_8\_TBW is

-- Port ( );

end DECODER\_3\_8\_TBW;

architecture Dataflow of DECODER\_3\_8\_TBW is

component DECODER\_3\_8\_DF is

Port ( IP : in STD\_LOGIC\_VECTOR (2 downto 0);

OP : out STD\_LOGIC\_VECTOR (7 downto 0));

end component;

Signal IP:STD\_LOGIC\_VECTOR(2 downto 0):="000";

Signal OP:STD\_LOGIC\_VECTOR(7 downto 0);

begin

UUT: DECODER\_3\_8\_DF Port map(IP=>IP, OP=>OP);

stim\_proc: process

begin

wait for 100ns;

IP(0)<='0';

IP(1)<='0';

IP(2)<='1';

wait for 100ns;

IP(0)<='0';

IP(1)<='1';

IP(2)<='0';

wait for 100ns;

IP(0)<='0';

IP(1)<='1';

IP(2)<='1';

```
wait for 100ns;
IP(0)<='1';
IP(1)<='0';
IP(2)<='0';
wait for 100ns;
IP(0)<='1';
IP(1)<='0';
IP(2)<='1';
wait for 100ns;
IP(0)<='1';
IP(1)<='1';
IP(2)<='0';
wait for 100ns;
IP(0)<='1';
IP(1)<='1';
IP(2)<='1';
wait;
end process;
end Dataflow;
```

## **TBW Waveform**

